

CS 211: Computer Architecture

Digital Logic

Topics:

- Converting truth tables to expressions
- Karnaugh maps

Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Given a circuit, isolate the rows in which the output of the circuit should be true

Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\bar{A}\bar{B}\bar{C} = 1$

$\bar{A}\bar{B}C = 1$

$A\bar{B}\bar{C} = 1$

$A\bar{B}C = 1$

$ABC = 1$

Given a circuit, isolate that rows in which the output of the circuit should be true

A product term that contains exactly one instance of every variable is called a minterm

Converting Truth Table to Boolean Expression

sensor inputs				
A	B	C	Output	
0	0	0	0	$\bar{A}\bar{B}\bar{C} = 1$
0	0	1	0	
0	1	0	0	
0	1	1	1	$A\bar{B}\bar{C} = 1$
1	0	0	0	$A\bar{B}C = 1$
1	0	1	1	
1	1	0	1	
1	1	1	1	$ABC = 1$

Output = $\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$

Given the expressions for each row, build a larger Boolean expression for the entire table.

- This is a **sum-of-products (SOP)** form.

Converting Truth Table to Boolean Expression

sensor inputs

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$\bar{A}BC = 1$$

$$A\bar{B}C = 1$$

$$ABC\bar{} = 1$$

$$ABC = 1$$

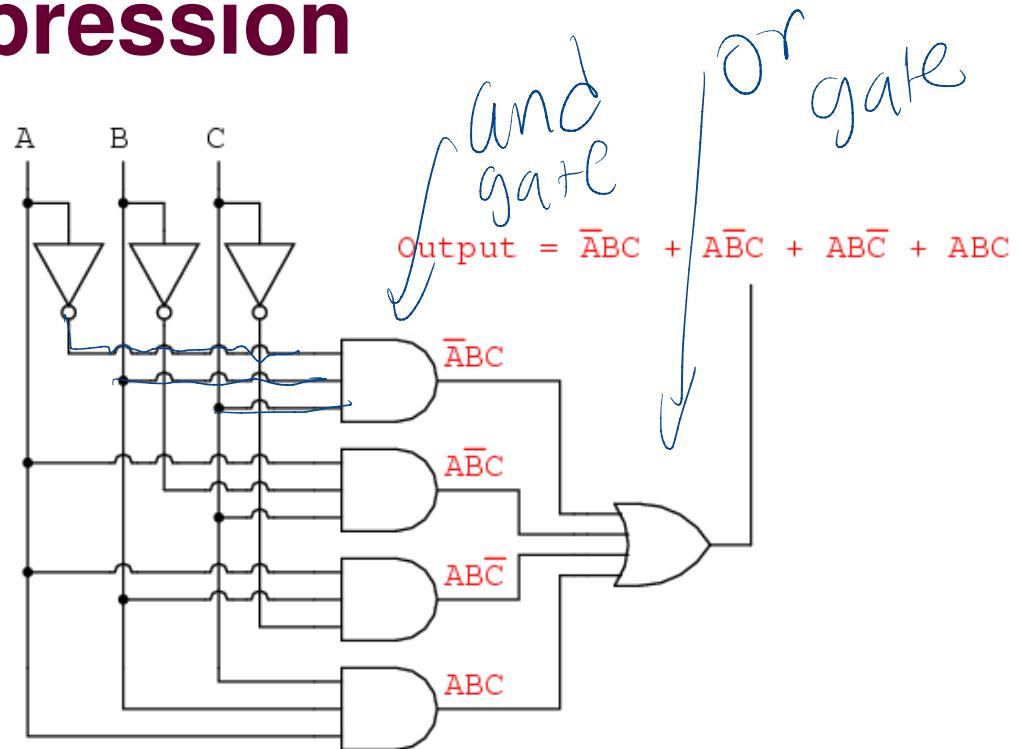
$$\text{Output} = \bar{A}BC + A\bar{B}C + ABC\bar{} + ABC$$





Finally build the circuit.

- Problem: SOP forms are often not minimal.
- Solution: Make it minimal. We'll go over two ways.

First approach: algebraic

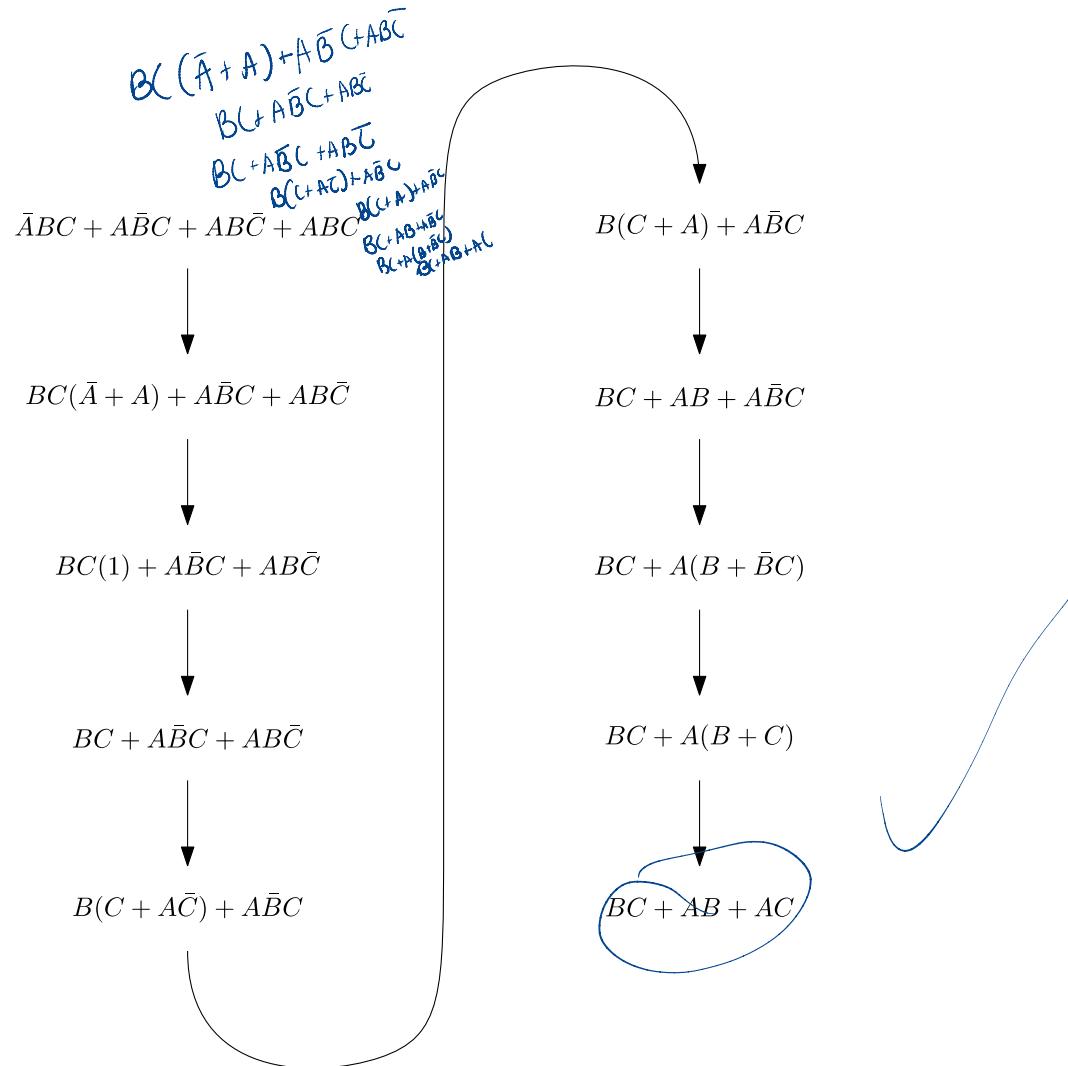

The Result

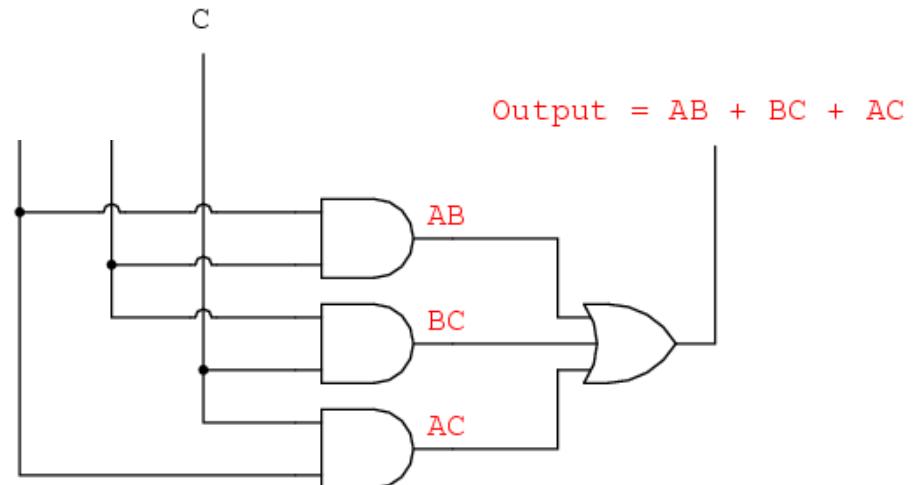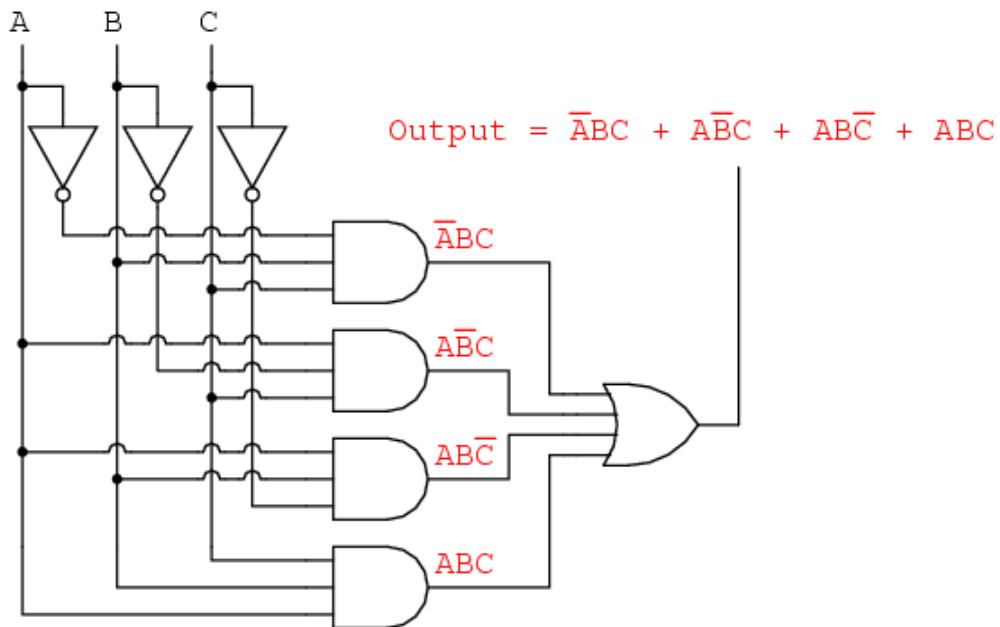


Karnaugh Maps or K-Maps




K-maps are a graphical technique to view minterms and how they relate.

The “map” is a diagram made up of squares, with each square representing a single minterm.



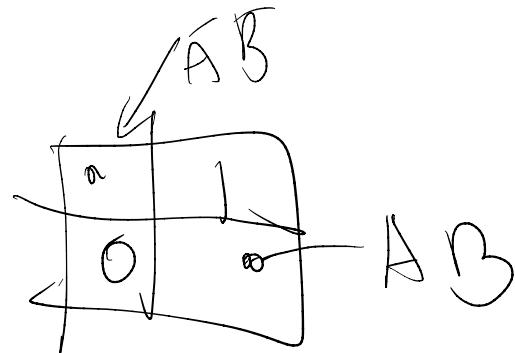
Minterms resulting in a “1” are marked as “1”, all others are marked “0”




2 Variable K-Map

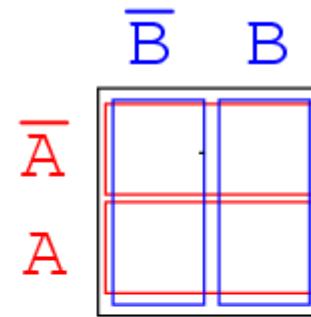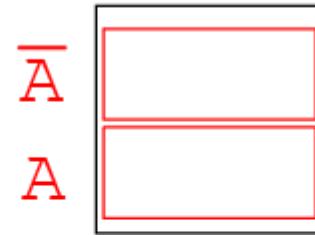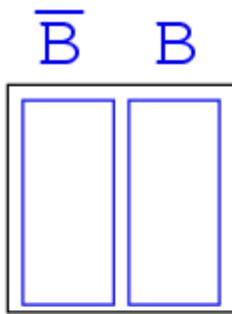




2 Variable K-Map

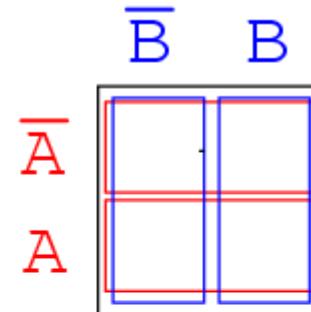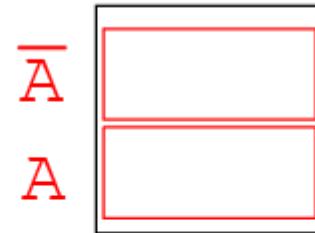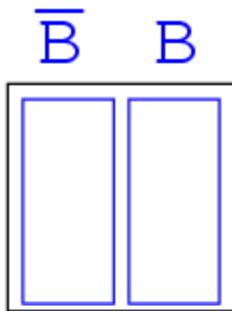

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

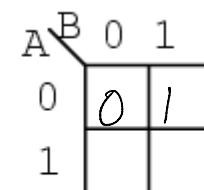

2 Variable K-Map

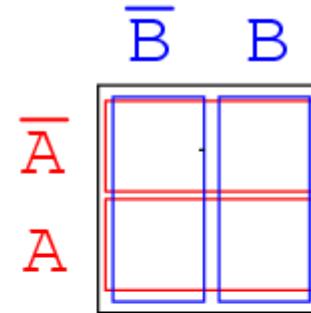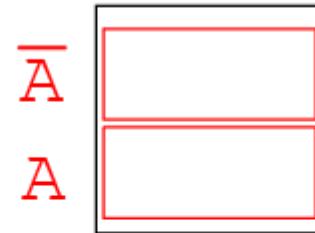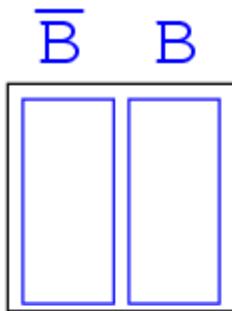


A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

A	B	0	1
0	0	0	1
1	0	0	1

Finding Commonality


$$\begin{array}{l}
 \overline{A}B + A\overline{B} \\
 = \overline{A}(B + \overline{B}) \\
 = \overline{A} \cdot 1 \\
 = \overline{A}
 \end{array}$$

Out = \overline{A}

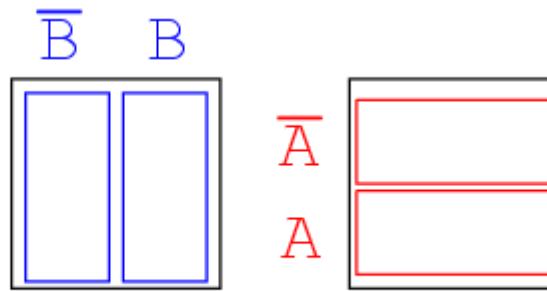

$$\begin{array}{l}
 \overline{A}\overline{B} + \overline{A}B \\
 = \overline{A}(\overline{B} + B) \\
 = \overline{A} \cdot 1 \\
 = \overline{A}
 \end{array}$$

Out = \overline{A}

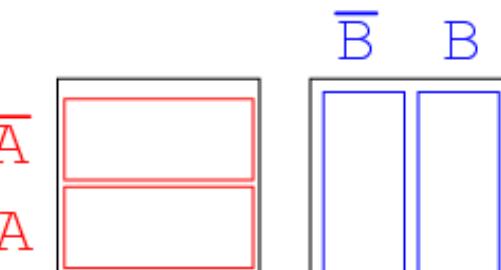

Finding the “best” solution

$$(A+B)(\bar{B}+B) = A+B$$

$A \oplus B$

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

Output = $A + B$



Wrong Output = $A\bar{B} + B$

$\bar{A}\bar{B} + AB$ $A(\bar{B}+B)$



Grouping become simplified products.

Both are “correct”. “ $A+B$ ” is preferred.


Simplify Example

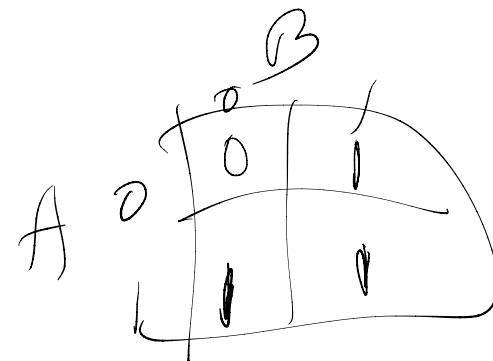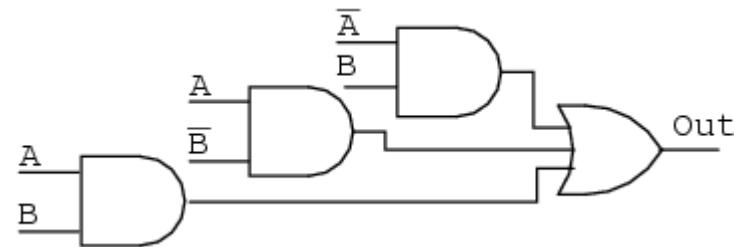

Simplify Example

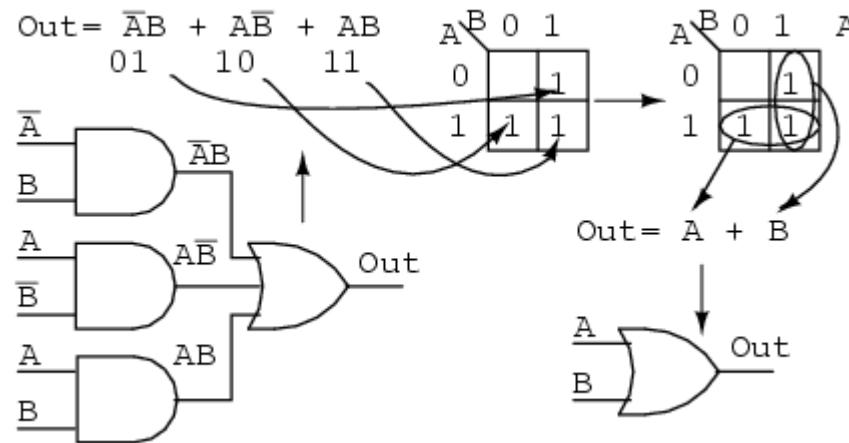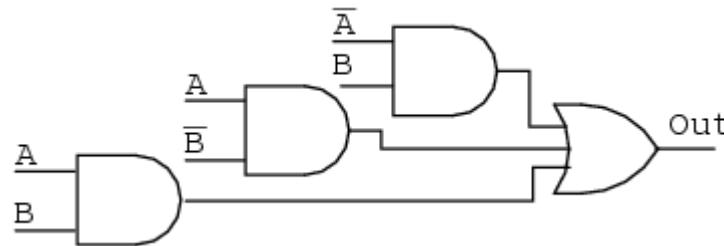

3 Variable K-Maps

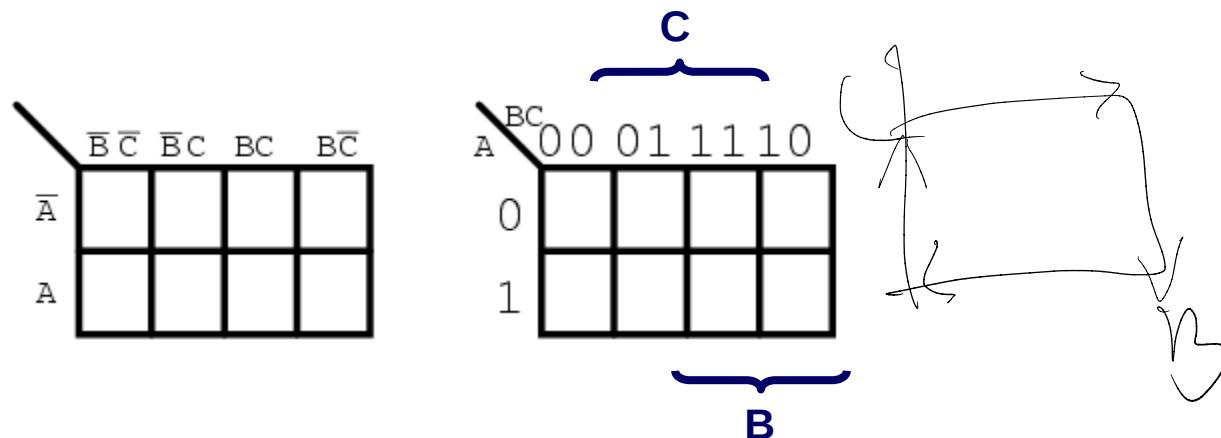

- Note in higher maps, several variables occupy a given axis
- The sequence of 1s and 0s follow a Gray Code Sequence.

3 Variable K-Maps

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}				
A				

	BC	00	01	11	10
A					
0		1	1	0	0
1		0	0	0	0

\bar{C}

$\bar{A} \bar{B} = 0$

$$\text{Out} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C = \bar{A}\bar{B}(\bar{C} + C) = \bar{A}\bar{B}$$

	BC	00	01	11	10
A					
0		1	1		
1					



$$\text{Out} = \bar{A}\bar{B}$$

\bar{A}

\bar{C}


\bar{C}

3 Variable K-Maps

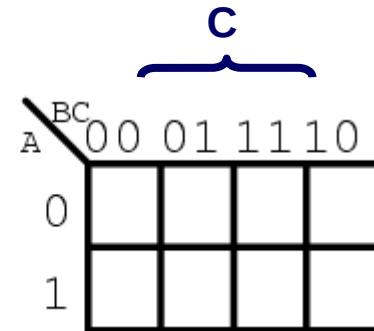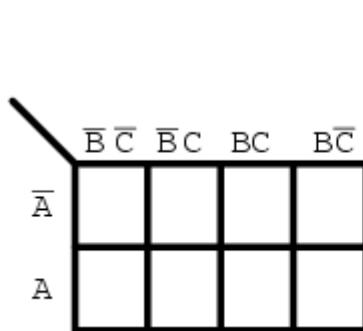

$$\bar{A}\bar{B} + \bar{A}B \\ \cancel{\bar{A}(B+B)}$$
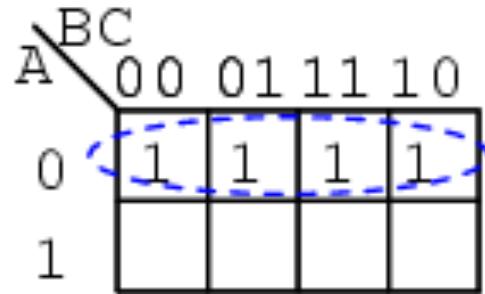
$$\text{Out} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$$





$$\bar{A}\bar{B} + \bar{A}B \\ \bar{A}(B+B)$$

$$\text{Out} = \bar{A}$$

3 Variable K-Maps

$\bar{A}C(\bar{B} + B)$

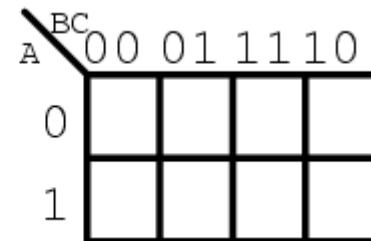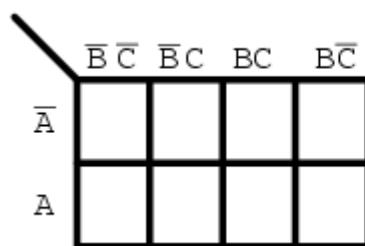


$\bar{A}C + \bar{A}C$

$C(\bar{A} + A)$



(C)
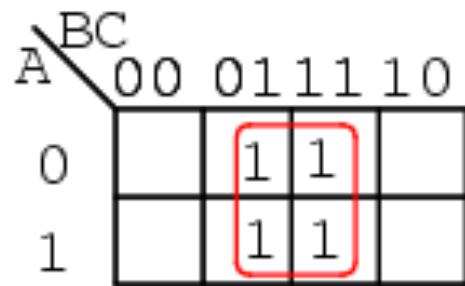
$$\text{Out} = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$




$$\text{Out} = C$$

3 Variable K-Maps

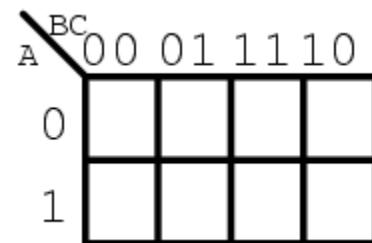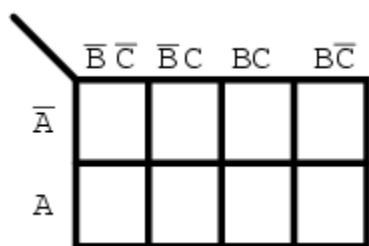

$$\begin{aligned} & A + \bar{A}B \\ & (\bar{A} + B)(A + \bar{A}) \end{aligned}$$
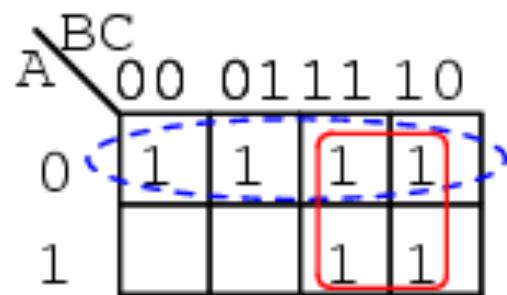
$$\text{Out} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + \bar{A}B\bar{C} + ABC + AB\bar{C}$$





$$\begin{aligned} & \bar{A}\bar{B} + \bar{A}B + A\bar{B} \\ & A\bar{B} + AB + \bar{A}B \end{aligned}$$

$$A(\bar{B} + B) \times \bar{F}B$$



$$\text{Out} = \bar{A} + B$$

$$A(\bar{B} + B) \times \bar{F}B$$


3 Variable K-Maps

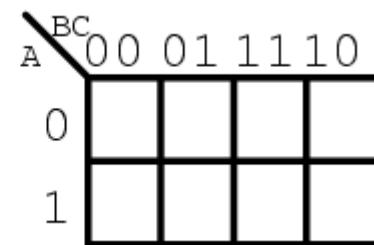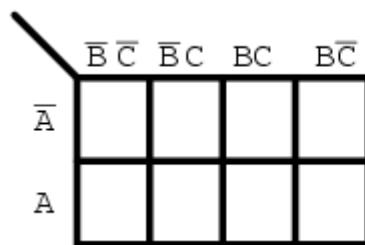
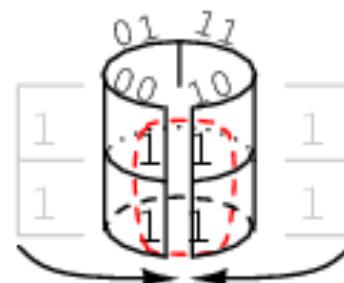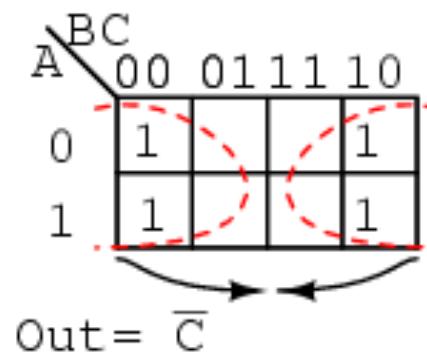
$$\text{Out} = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C}$$




Back to our earlier example.....


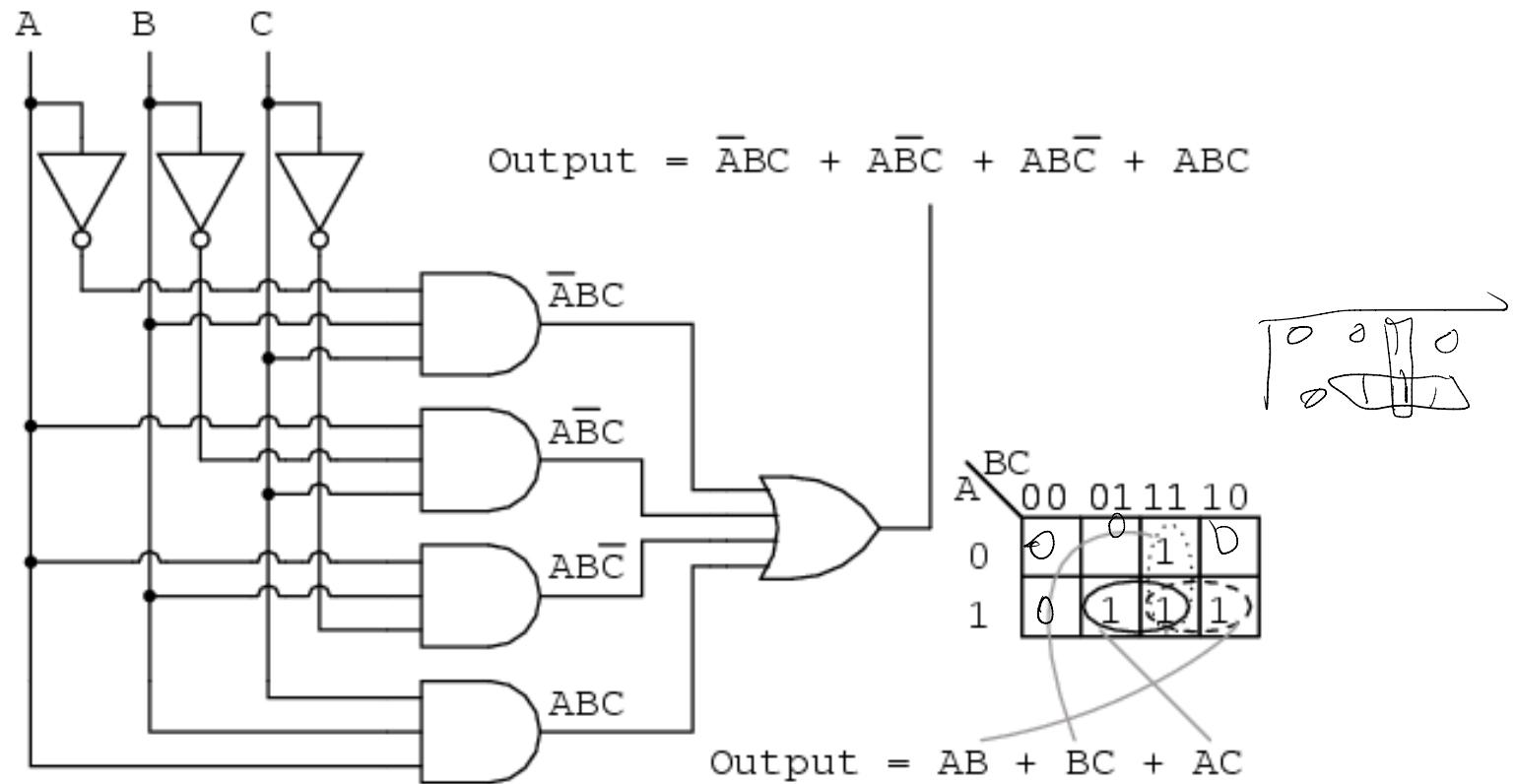


The K-map and the algebraic produce the same result.

Up... up... and let's keep going


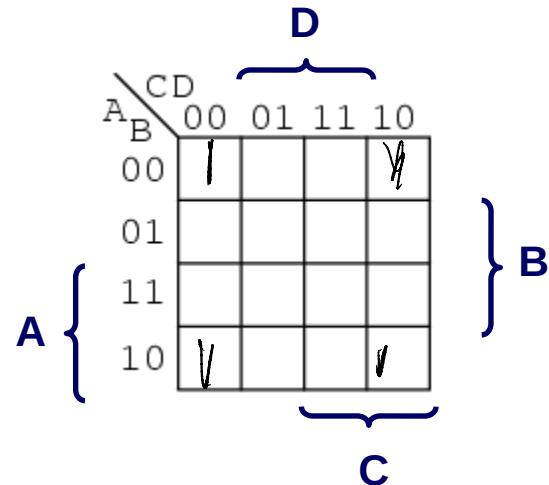

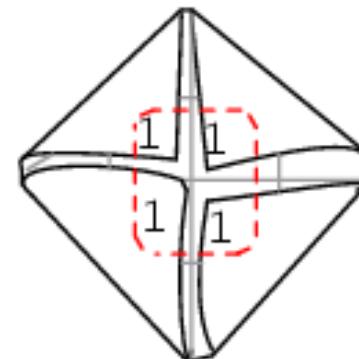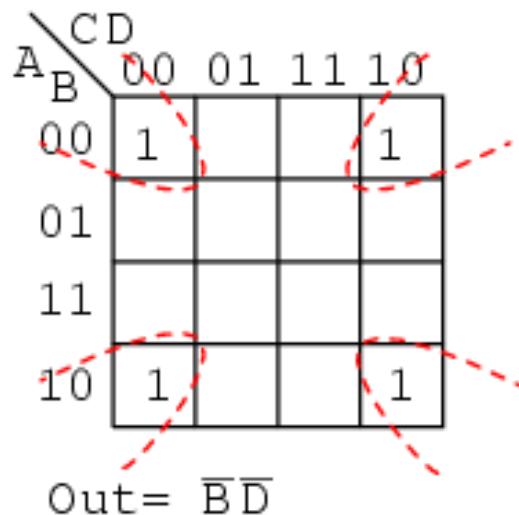
$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$




$$\text{Out} = \overline{B}\overline{D}$$

Few more examples

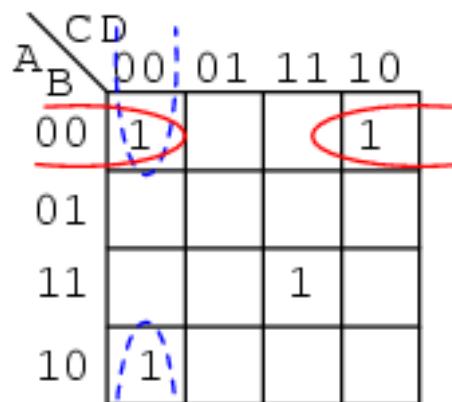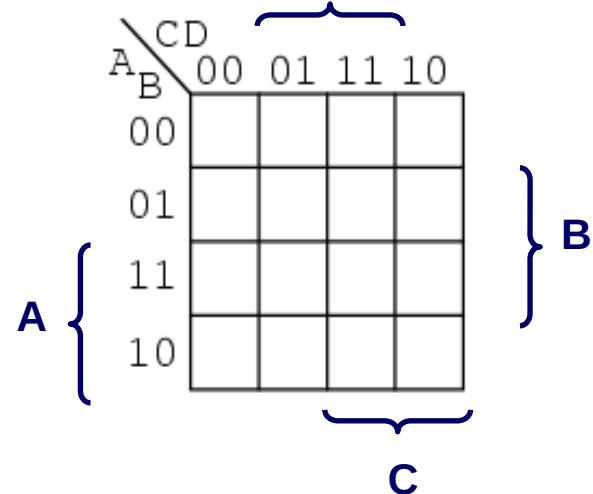

Out = $\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{D} + ABCD$

Few more examples

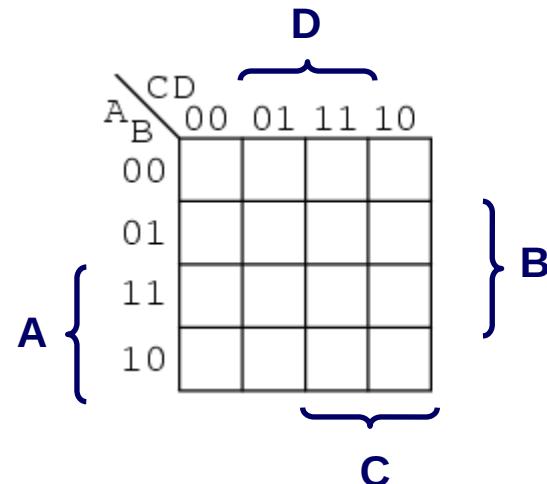

$$\text{Out} = \overline{ABC}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}\overline{C}\overline{D}$$

$$+ \overline{A}\overline{B}CD + \overline{AB}\overline{C}D + \overline{AB}\overline{C}\overline{D}$$

$$+ ABC\overline{D} + AB\overline{C}D + ABCD$$

	CD	00	01	11	10
A					
B					
00		1	1		
01		1	1	1	
11		1	1	1	
10					

	CD	00	01	11	10
A					
B					
00		1	1	1	
01		1	1	1	
11		1	1	1	
10					

	CD	00	01	11	10
A					
B					
00		1	1	1	
01		1	1	1	
11		1	1	1	
10					

$$\text{Out} = \overline{AC} + \overline{AD} + B\overline{C} + BD$$

Don't Care Conditions

- Let $F = AB + \bar{A}\bar{B}$
- Suppose we know that a disallowed input combo is $A=1, B=0$
- Can we replace F with a simpler function G whose output matches for all inputs we do care about?
- Let H be the function with Don't-care conditions for obsolete inputs

Inputs will not occur 

A	B	F	H	G
0	0	1	1	1
0	1	0	0	0
1	0	0	X	1
1	1	1	1	1

$G = AB + \bar{B}$

- Both F & G are appropriate functions for H
- G can substitute for F for valid input combinations

Don't Cares can Greatly Simplify Circuits

Sometimes “don’t cares” greatly simplify circuitry

A Karnaugh map for a four-variable function (A, B, C, D) is shown. The variables are labeled A (bottom-left), B (middle-right), C (bottom-right), and D (top). The map consists of four columns and four rows. The top row contains 1, X, X, X. The second row contains X, 1, X, X. The third row contains 0, 0, 1, X. The bottom row contains 0, 0, X, 1. The variable D is written above the first column.

1	X	X	X
X	1	X	X
0	0	1	X
0	0	X	1

Below the Karnaugh map is a simplified expression:

$$\overline{ABCD} + \overline{ABC}\bar{D} + ABCD + A\overline{BCD}$$

vs.

$$\overline{A} + C$$

$$\overline{ABCD} + \overline{ABC}\bar{D} + ABCD + A\overline{BCD} \text{ vs. } \overline{A} + C$$

Formal Definition of Minterms

e.g., Minterms for 3 variables A,B,C

A	B	C	minterm
0	0	0	$m_0 \bar{A}\bar{B}\bar{C}$
0	0	1	$m_1 \bar{A}\bar{B}C$
0	1	0	$m_2 \bar{A}BC$
0	1	1	$m_3 \bar{A}B\bar{C}$
1	0	0	$m_4 A\bar{B}\bar{C}$
1	0	1	$m_5 A\bar{B}C$
1	1	0	$m_6 AB\bar{C}$
1	1	1	$m_7 ABC$

- A product term in which all variables appear once, either complemented or uncomplemented (i.e., an entry in the truth table).
- Each minterm evaluates to 1 for exactly one variable assignment, 0 for all others.
- Denoted by m_X where X corresponds to the variable assignment for which $m_X = 1$.

Minterm Example

A	B	C	F	\bar{F}	minterm
0	0	0	1	0	$m_0 \bar{A}\bar{B}\bar{C}$
0	0	1	1	0	$m_1 \bar{A}\bar{B}C$
0	1	0	1	0	$m_2 \bar{A}B\bar{C}$
0	1	1	0	1	$m_3 \bar{A}BC$
1	0	0	1	0	$m_4 A\bar{B}\bar{C}$
1	0	1	1	0	$m_5 A\bar{B}C$
1	1	0	0	1	$m_6 AB\bar{C}$
1	1	1	0	1	$m_7 ABC$


(variables appear once in each minterm)

$$\begin{aligned} F &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} \\ &= m_0 + m_1 + m_2 + m_4 + m_5 \\ &= \sum m(0,1,2,4,5) \end{aligned}$$

$$\begin{aligned} \bar{F} &= \bar{A}BC + AB\bar{C} + ABC \\ &= m_3 + m_6 + m_7 \\ &= \sum m(3,6,7) \end{aligned}$$

Minterm Example

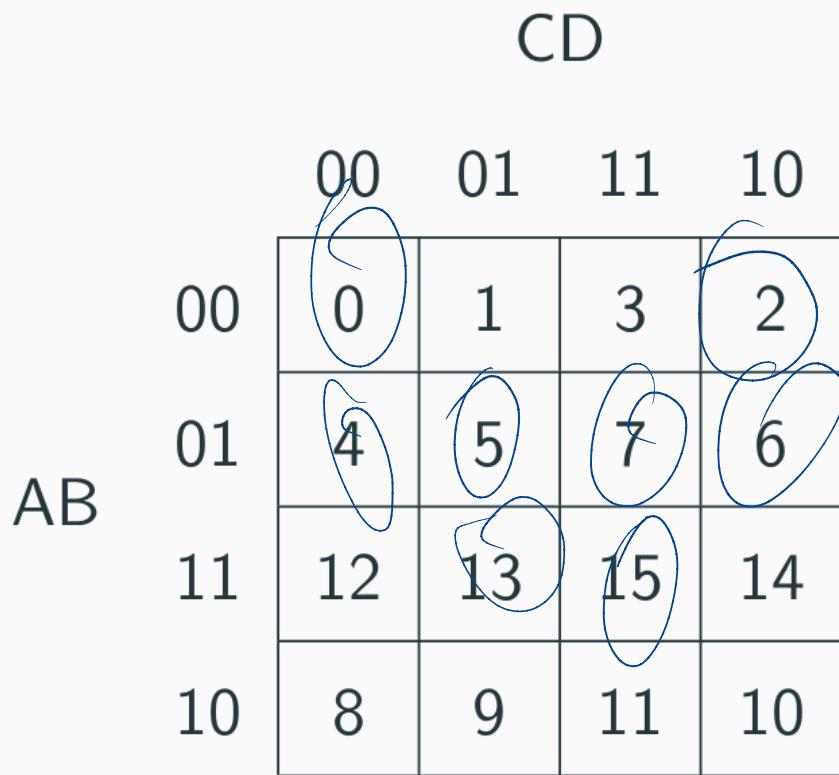Circuits may be specified in the form $\sum m(0, 2, 4, 5, 6, 7, 13, 15)$, where the indices correspond to positions in a Karnaugh map:



Minterm Example

Circuits may be specified in the form $\sum m(0, 2, 4, 5, 6, 7, 13, 15)$, where the indices correspond to positions in a Karnaugh map:

		CD				
		00	01	11	10	
AB		00	1	0	0	1
		01	1	1	1	1
		11	0	1	1	0
		10	0	0	0	0

Formal Definition of Maxterms

A	B	C		maxterm
0	0	0	M0	$A+B+C$
0	0	1	M1	$A+B+\bar{C}$
0	1	0	M2	$A+\bar{B}+C$
0	1	1	M3	$A+\bar{B}+\bar{C}$
1	0	0	M4	$\bar{A}+B+C$
1	0	1	M5	$\bar{A}+B+\bar{C}$
1	1	0	M6	$\bar{A}+\bar{B}+C$
1	1	1	M7	$\bar{A}+\bar{B}+\bar{C}$

- A sum term in which all variables appear once, either complemented or uncomplemented.
- Each maxterm evaluates to 0 for exactly one variable assignment, 1 for all others.
- Denoted by MX where X corresponds to the variable assignment for which $MX = 0$.

Maxterm Example

A	B	C	maxterm	F	
0	0	0	M0 $A+B+C$	1	
0	0	1	M1 $A+B+\bar{C}$	1	$F = (A+\bar{B}+\bar{C}) (\bar{A}+\bar{B}+C) (\bar{A}+\bar{B}+\bar{C})$
0	1	0	M2 $A+\bar{B}+C$	1	$= (M3) (M6) (M7)$
0	1	1	M3 $A+\bar{B}+\bar{C}$	0	$= \prod M(3,6,7)$
1	0	0	M4 $\bar{A}+B+C$	1	
1	0	1	M5 $\bar{A}+B+\bar{C}$	1	
1	1	0	M6 $\bar{A}+\bar{B}+C$	0	
1	1	1	M7 $\bar{A}+\bar{B}+\bar{C}$	0	

Maxterm Example

Then we can find the usual sum of products:

		CD				
		00	01	11	10	
AB		00	1	0	0	1
		01	1	1	1	1
		11	0	1	1	0
		10	0	0	0	0

$$F = BD + \bar{A}\bar{D}$$

$$\begin{aligned} & \bar{A}\bar{C}\bar{D} + B + \bar{B}D \\ & + \bar{A}C\bar{D} \end{aligned}$$

$$\bar{A}\bar{D} + B D$$

$$\bar{A}(\bar{B}D + C)$$

Maxterm Example


Or the product of sums:

		CD	
		00	01
		11	10
AB			
00	1	0	0
01	1	1	1
11	0	1	1
10	0	0	0

$$F = (\bar{A} + D)(B + \bar{D})$$

A handwritten diagram showing the decomposition of the function F . It consists of two parts: $\bar{A} + D$ and $B + \bar{D}$. The first part, $\bar{A} + D$, is shown with a blue bracket spanning the columns for CD values 00 and 01, and another blue bracket spanning the rows for AB values 11 and 10. The second part, $B + \bar{D}$, is shown with a green bracket spanning the columns for CD values 00 and 10, and another green bracket spanning the rows for AB values 00 and 11.

Converting Between Canonical Forms

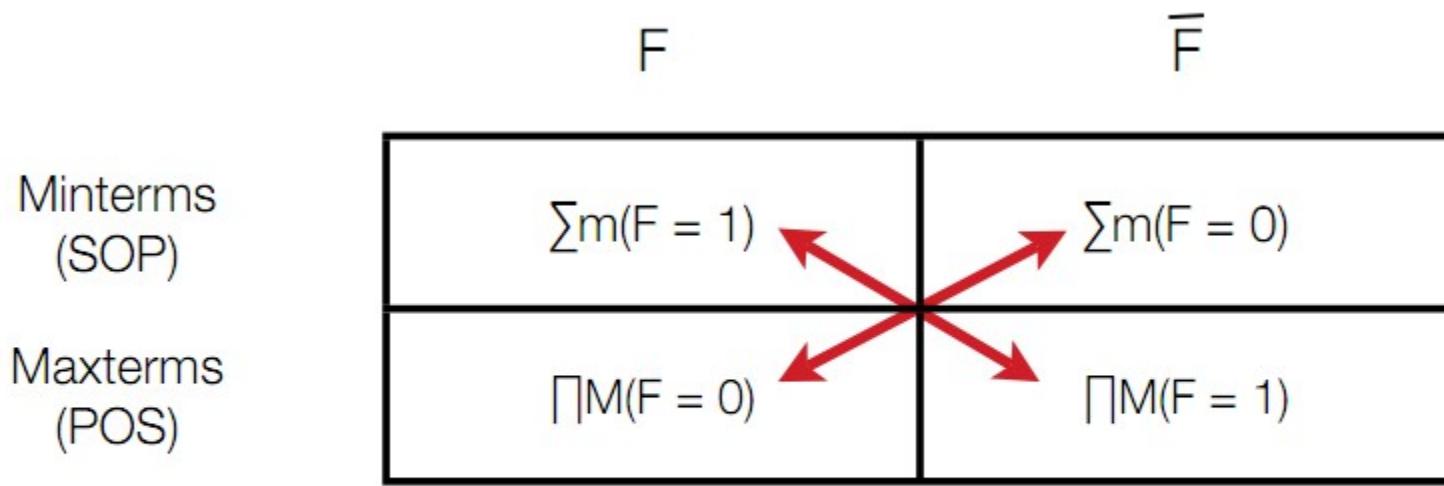

DeMorgans: same terms

Product of Sums Example

WX \ YZ	00	01	11	10
00	1	1	0	1
01	1	0	0	0
11	1	0	0	0
10	1	1	0	1



$$\bar{F} = YZ + XZ + YX$$

DeMorgan's

$$F = (\bar{Y}+\bar{Z})(\bar{Z}+\bar{X})(\bar{Y}+\bar{X})$$



K-maps and Implicants

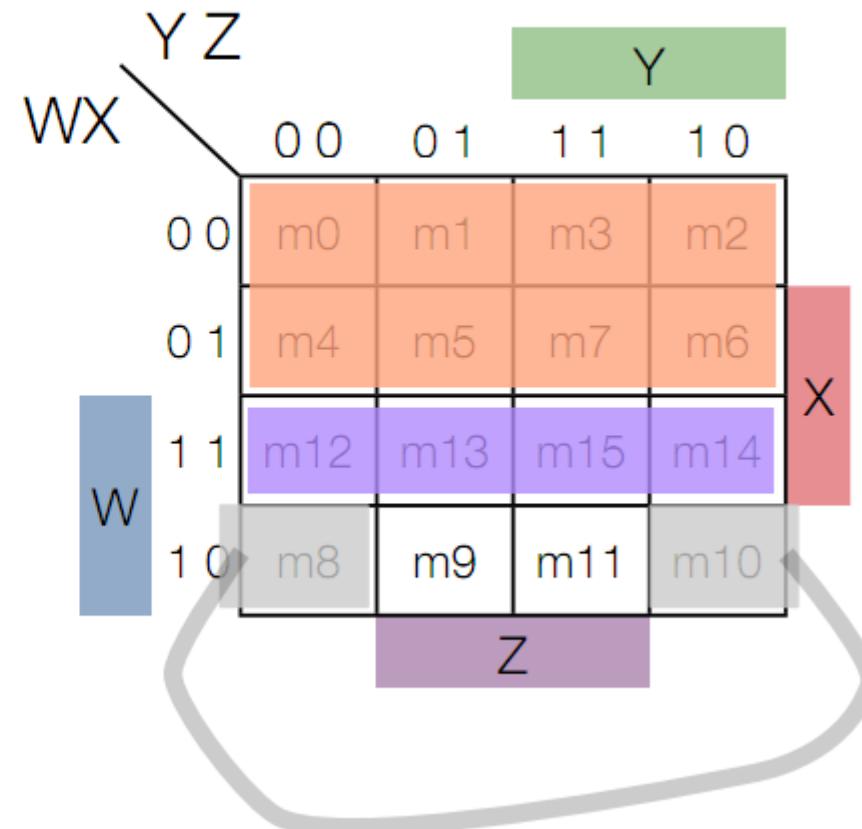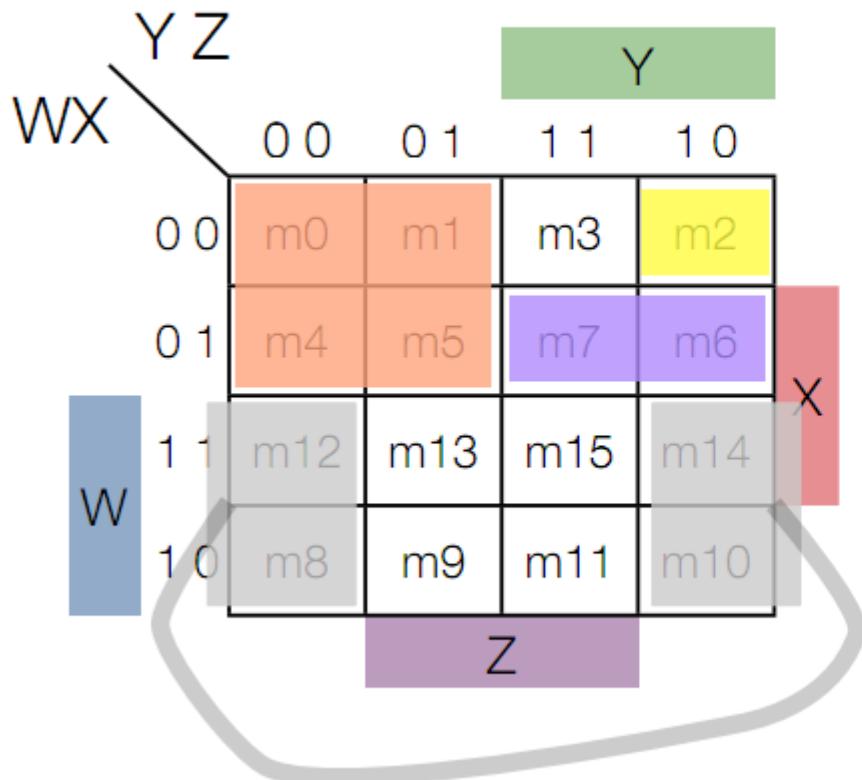- **Implicant:** a product term, which, viewed in a K-Map is a $2^i \times 2^j$ size “rectangle” (possibly wrapping around) where $i=0,1,2$, $j=0,1,2$



Implicants

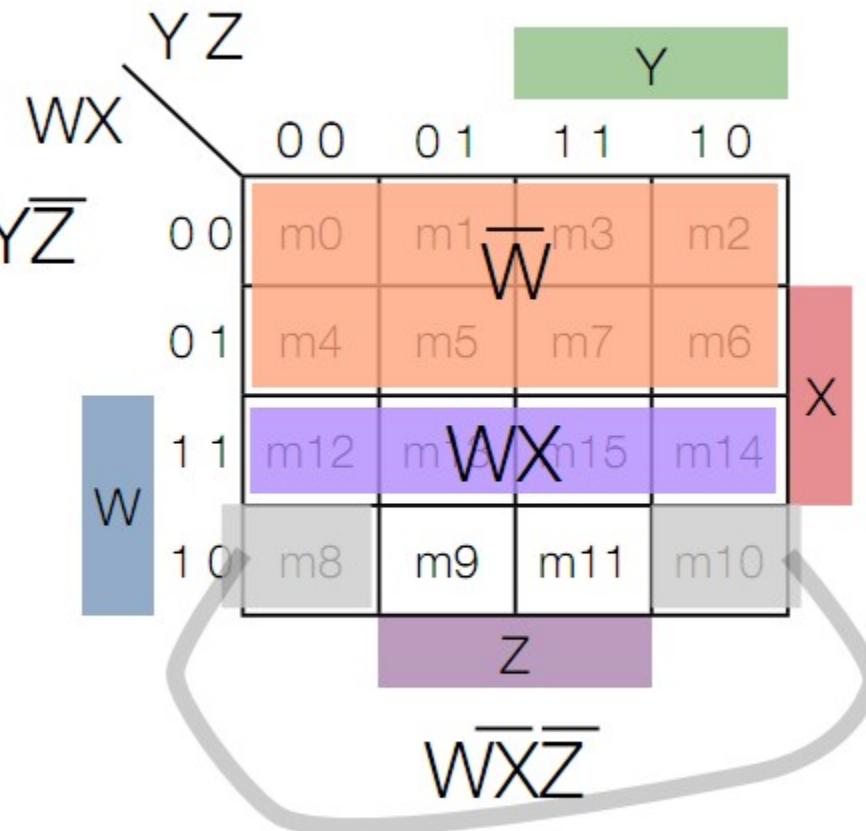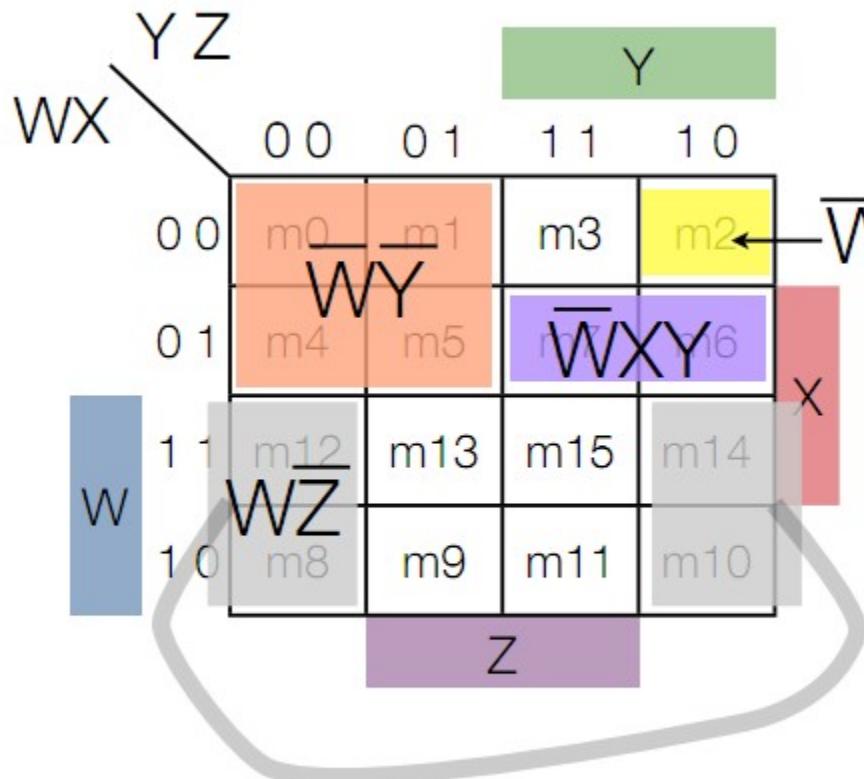- **Implicant:** a product term, which, viewed in a K-Map is a $2^i \times 2^j$ size “rectangle” (possibly wrapping around) where $i=0,1,2$, $j=0,1,2$



Note: bigger rectangles = fewer literals


More Implicant Terminology

Implicant: product term, which when viewed in a K-map, is a rectangle of 1s

Prime implicant: an implicant not contained in another implicant




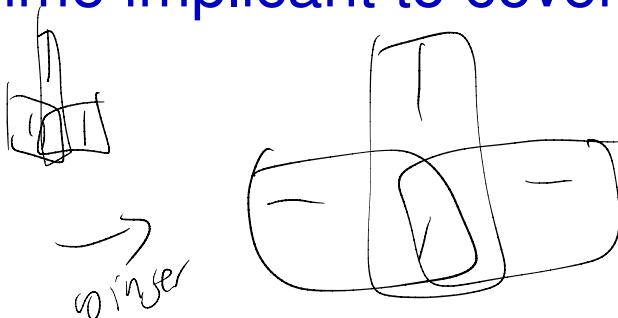Essential prime implicant: a prime implicant that is the only prime implicant to cover some minterm



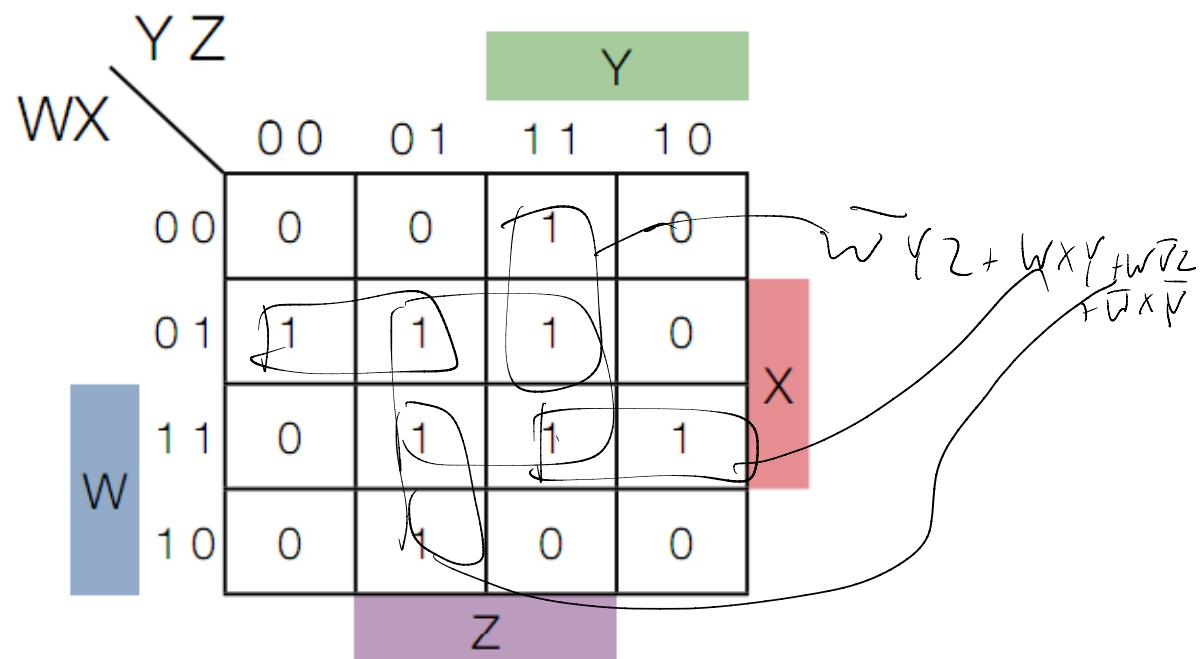Example

- List all of the prime implicants for this function
- Is any of them an essential prime implicant?
- What is a simplified expression for this function?



Example

- Step 1: Identify all PIs and essential PIs
- Step 2: Include all Essential PIs in the circuit (Why?)
- Step 3: If any 1-valued minterms are uncovered by EPIs, choose PIs that are “big” and do a good job covering
- Selection Rule: a heuristic for usually choosing “good” PIs: choose the PIs that minimize overlap with one another and with EPIs

Red bounds are EPIs (solo-covered minterm shown in red)

1	1	0	0
0	1	1	1
1	1	1	1
1	1	0	0


Also need
(purple or blue) and
(yellow or green)

All blue PIs or all
green PIs cover

No EPIs!

1	1	0	0
0	1	1	0
0	0	1	1
1	0	0	1


Design Example

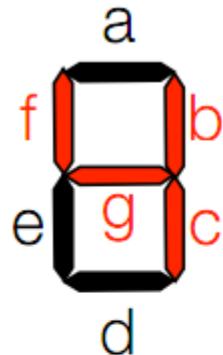


e.g., what outputs
“lights up” when input
 $V=4$?

	Input											
Va	W	X	Y	Z	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	
1	0	0	0	1	0	1	1	0	0	0	0	
2	0	0	1	0	1	1	0	1	1	0	1	
3	0	0	1	1	1	1	1	1	0	0	1	
4	0	1	0	0	0	1	1	0	0	1	1	
5	0	1	0	1	1	0	1	1	0	1	1	
6	0	1	1	0	1	0	1	1	1	1	1	
7	0	1	1	1	1	1	1	0	0	0	0	
8	1	0	0	0	1	1	1	1	1	1	1	
9	1	0	0	1	1	1	1	0	0	1	1	
X	1	0	1	0	X	X	X	X	X	X	X	
X	1	0	1	1	X	X	X	X	X	X	X	
X	1	1	0	0	X	X	X	X	X	X	X	
X	1	1	0	1	X	X	X	X	X	X	X	
X	1	1	1	0	X	X	X	X	X	X	X	
X	1	1	1	1	X	X	X	X	X	X	X	

Design Example

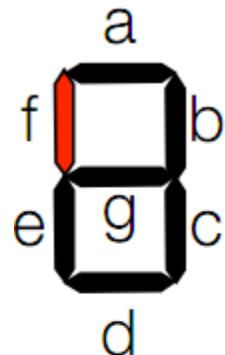

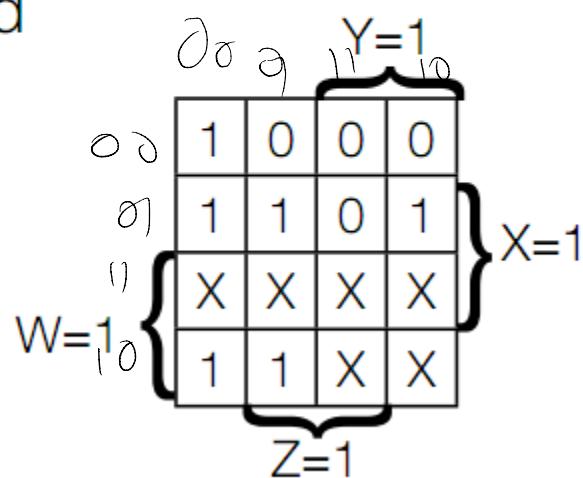For what values does output f "light up" for?



Input Output

Va	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	1	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	0	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Design Example

