

CS 211: Computer Architecture

Digital Logic

Topics:

- Transistors
- Logic Gates
- Boolean algebra

Transistor: Building Block of Computers

Microprocessors contain millions (billions) of transistors

- Intel Pentium 4 (2000): 48 million
- IBM PowerPC 750FX (2002): 38 million
- IBM/Apple PowerPC G5 (2003): 58 million

Logically, each transistor acts as a switch


Combined to implement logic functions

- AND, OR, NOT


Combined to build higher-level structures

- Adder, multiplexer, decoder, register, ...

Combined to build processor

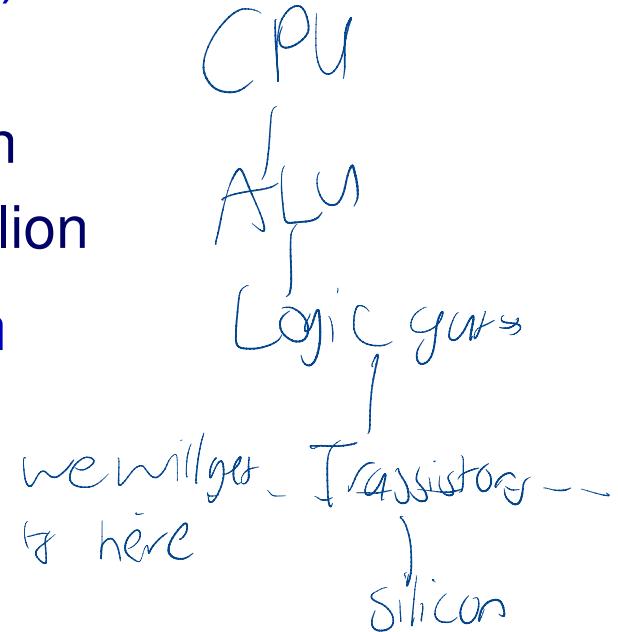

Simple Switch Circuit

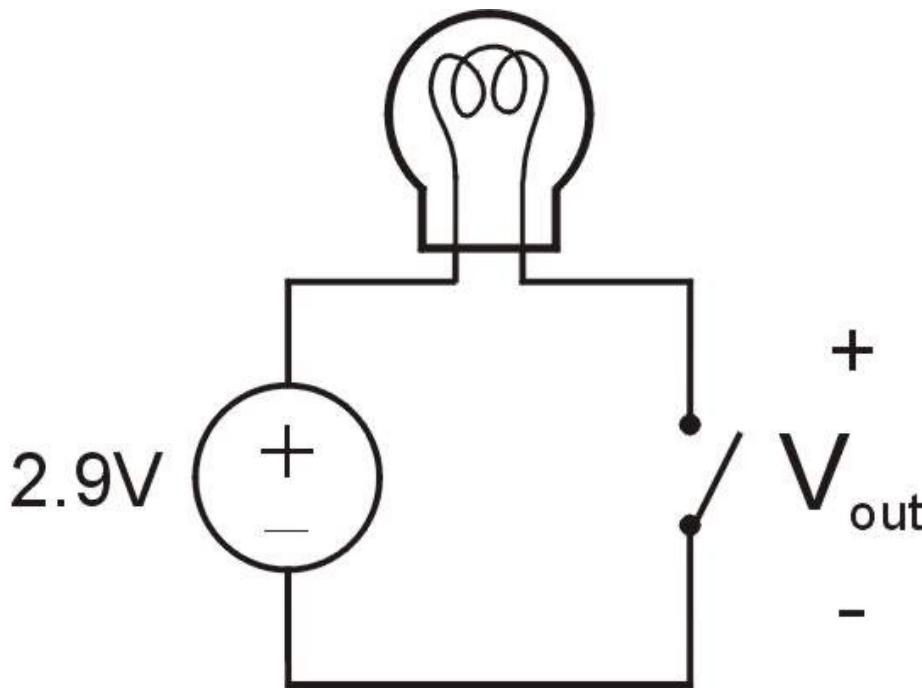

Switch open:

- No current through circuit
- Light is off
- V_{out} is +2.9V

Switch closed:

- Current flows
- Light is on
- V_{out} is 0V

Switch-based circuits can easily represent two states:
on/off, open/closed, voltage/no voltage.


n-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: n-type and p-type

n-type

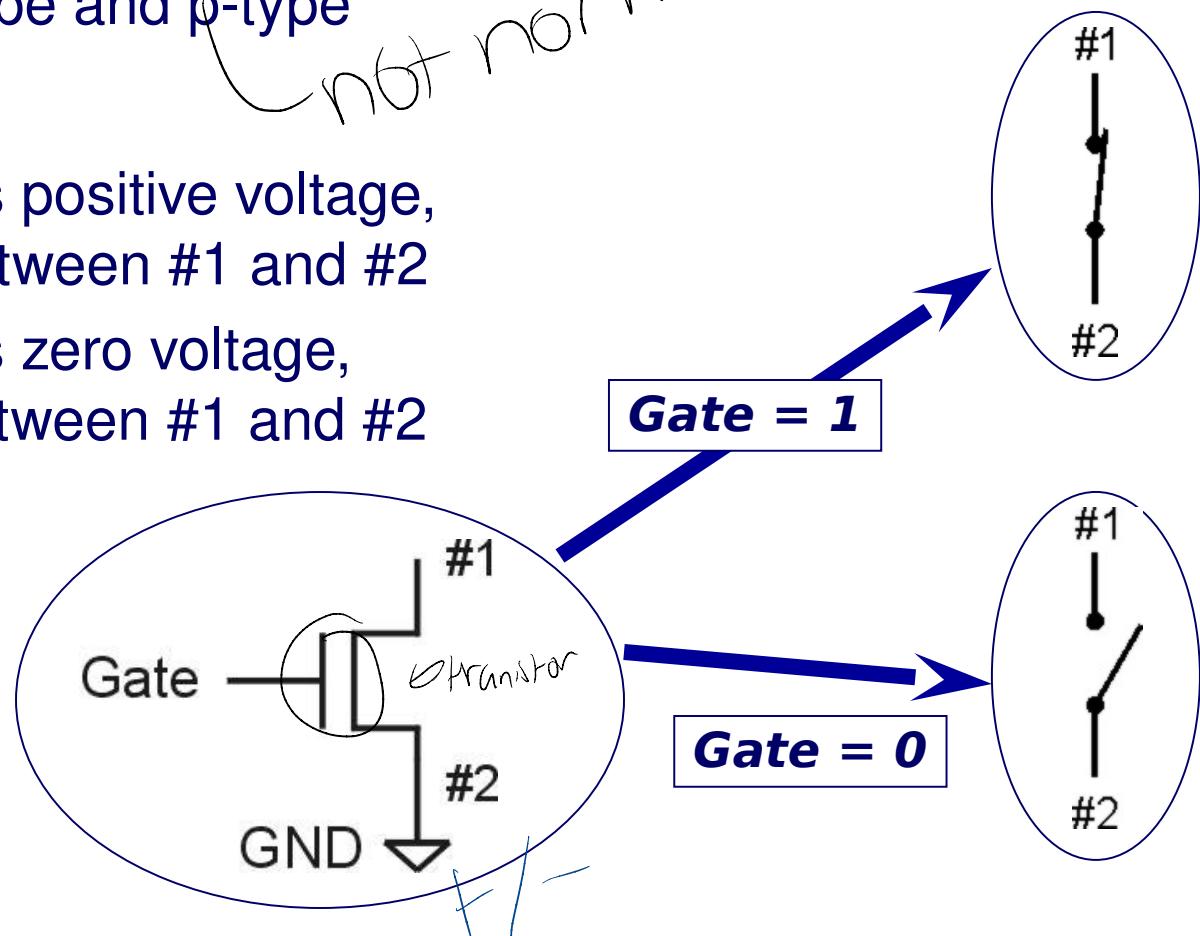
- when Gate has positive voltage, short circuit between #1 and #2
- when Gate has zero voltage, open circuit between #1 and #2



p-type MOS Transistor

p-type is complementary to n-type

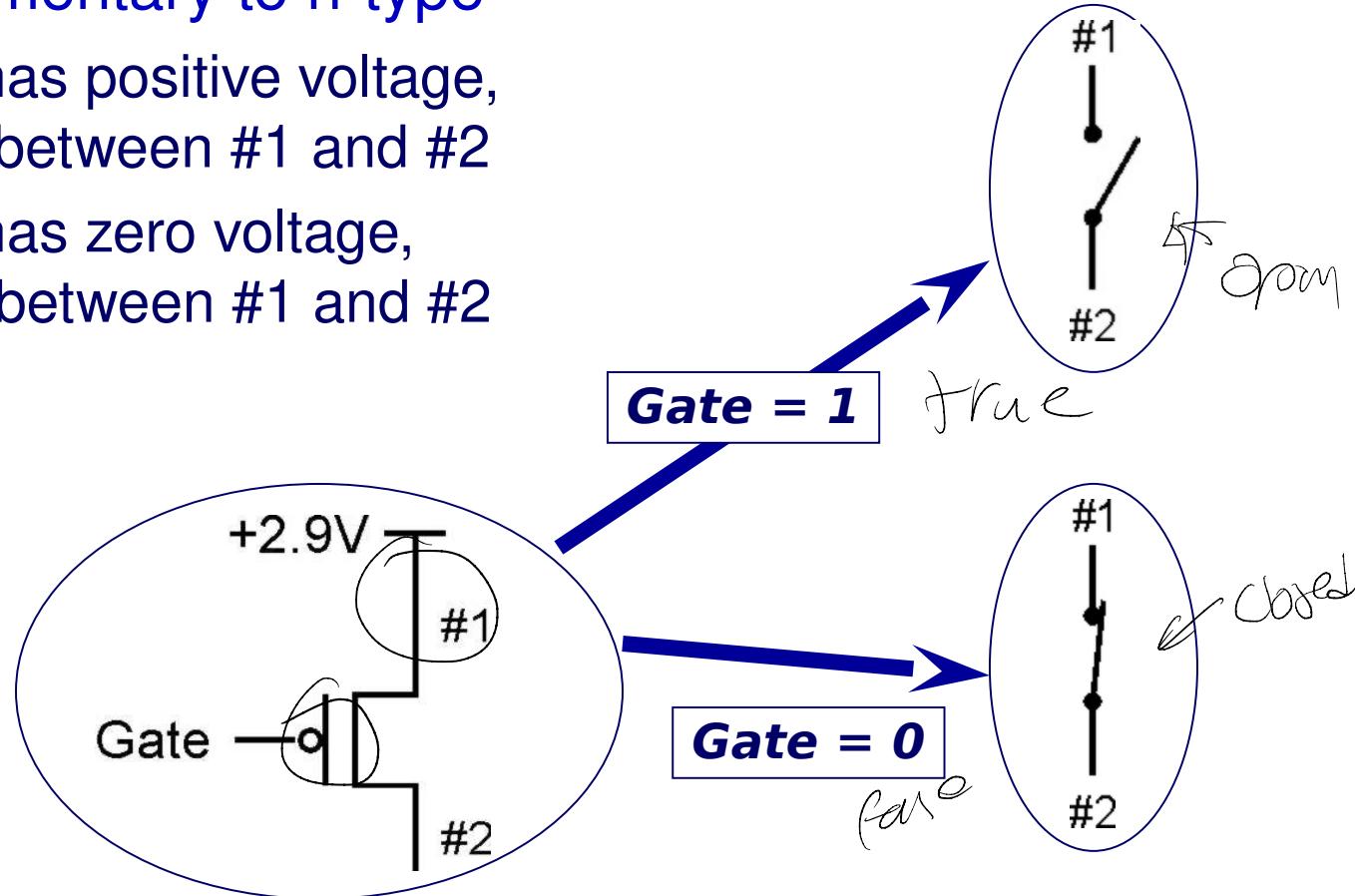- when Gate has positive voltage, open circuit between #1 and #2
- when Gate has zero voltage, short circuit between #1 and #2




Logic Gates

Use transistors to implement logical functions: AND, OR, NOT

Digital symbols:

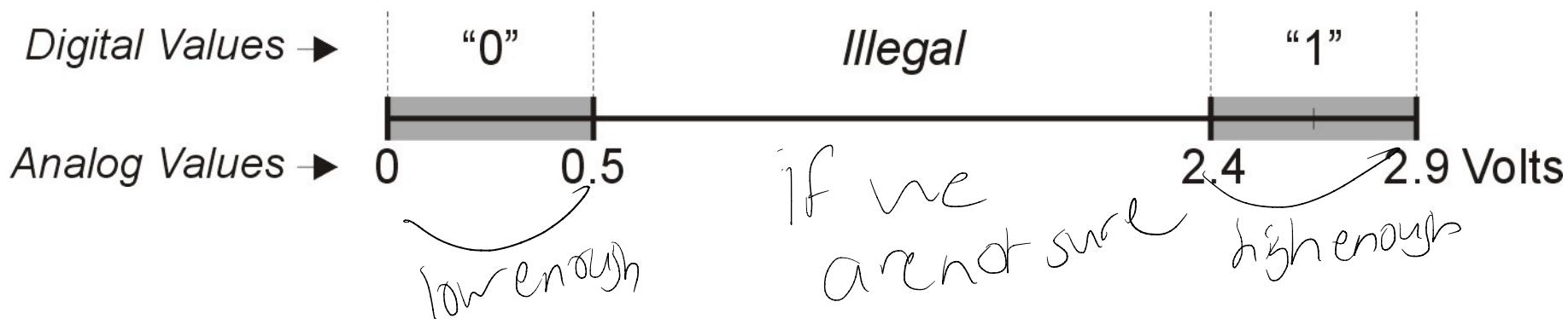- recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
 - typical values for "1": +5V, +3.3V, +2.9V
 - from now on we'll use +2.9V

CMOS Circuit


Complementary MOS

Uses both n-type and p-type MOS transistors


- p-type
 - Attached to + voltage
 - Pulls output voltage UP when input is zero
- n-type
 - Attached to GND
 - Pulls output voltage DOWN when input is one

MOS transistors are combined to form Logic Gates

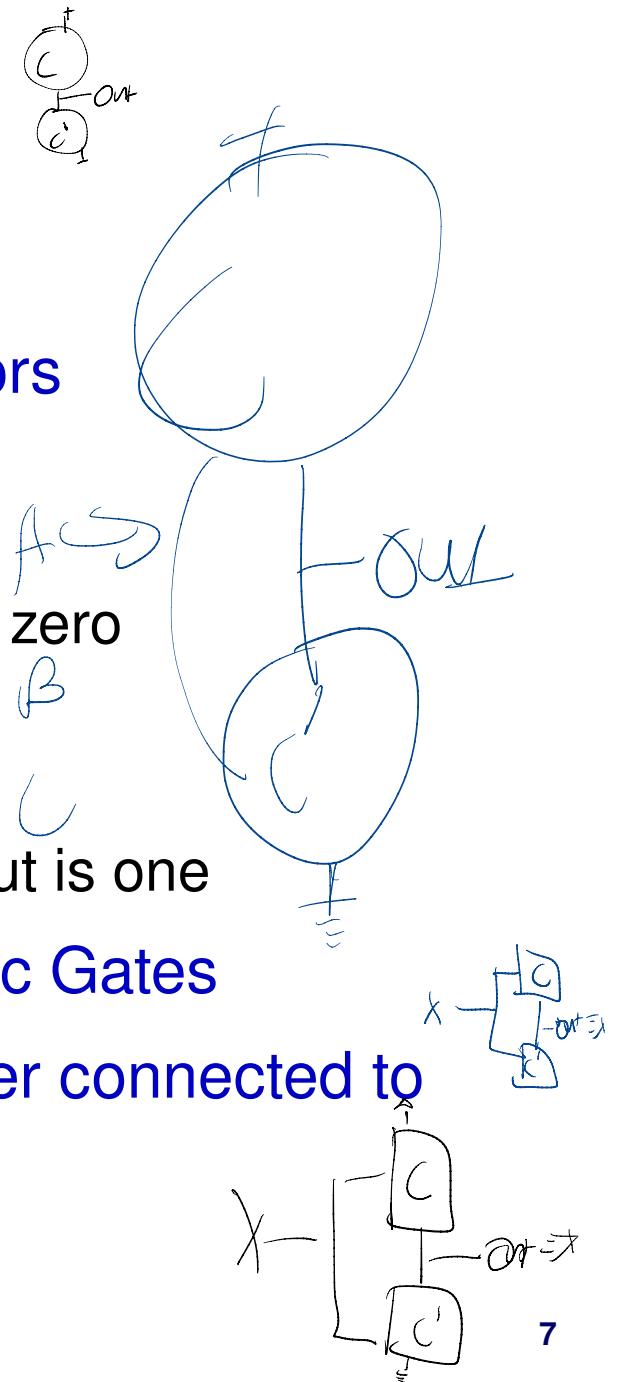For all inputs, make sure that output is either connected to GND or to +, but not both!




Inverter (NOT Gate)


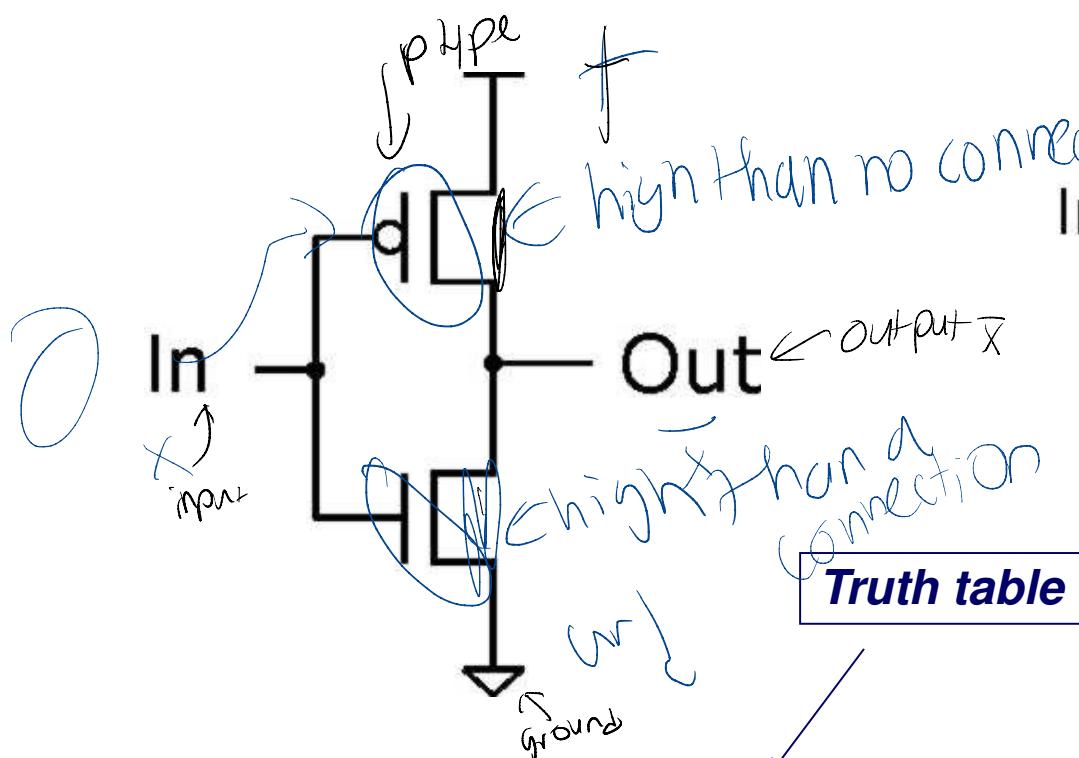


In	Out
0 V	2.9 V
2.9 V	0 V

In	Out
0	1
1	0

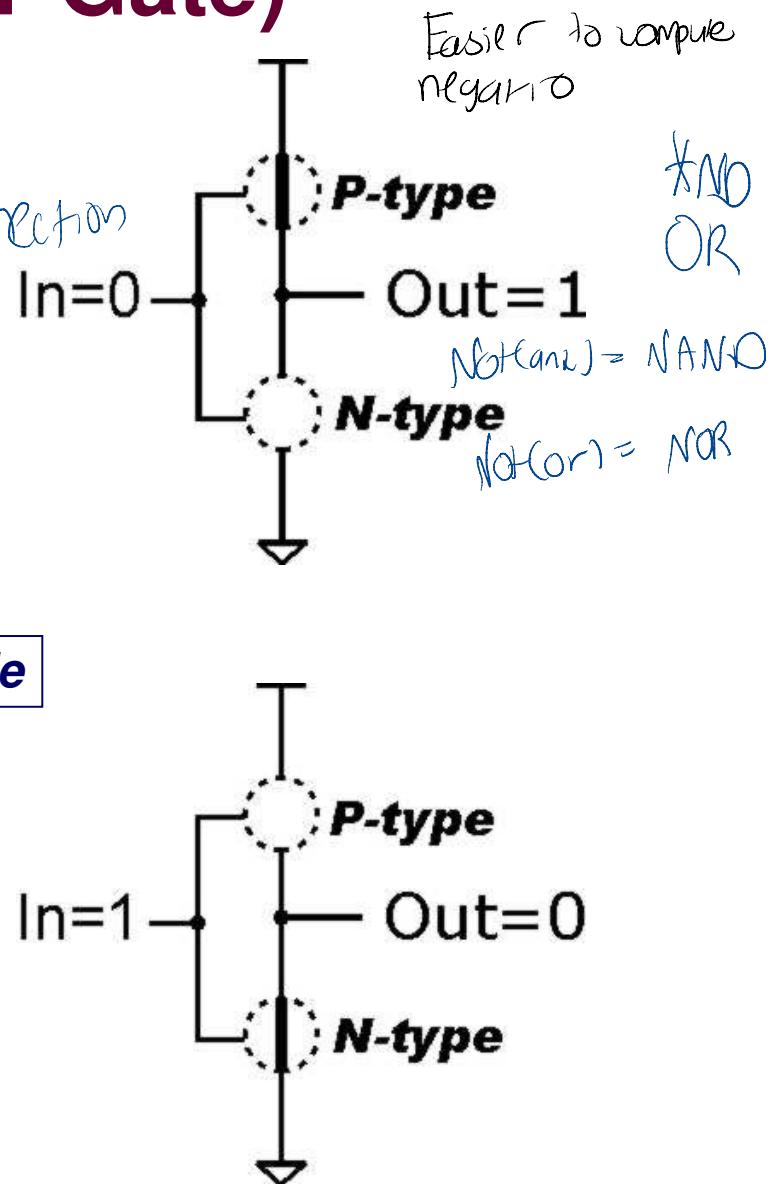


NOR Gate

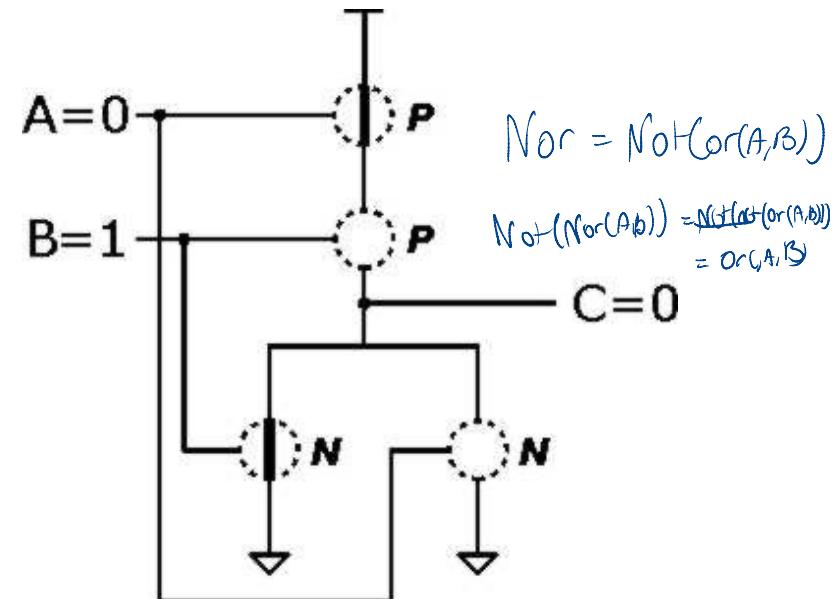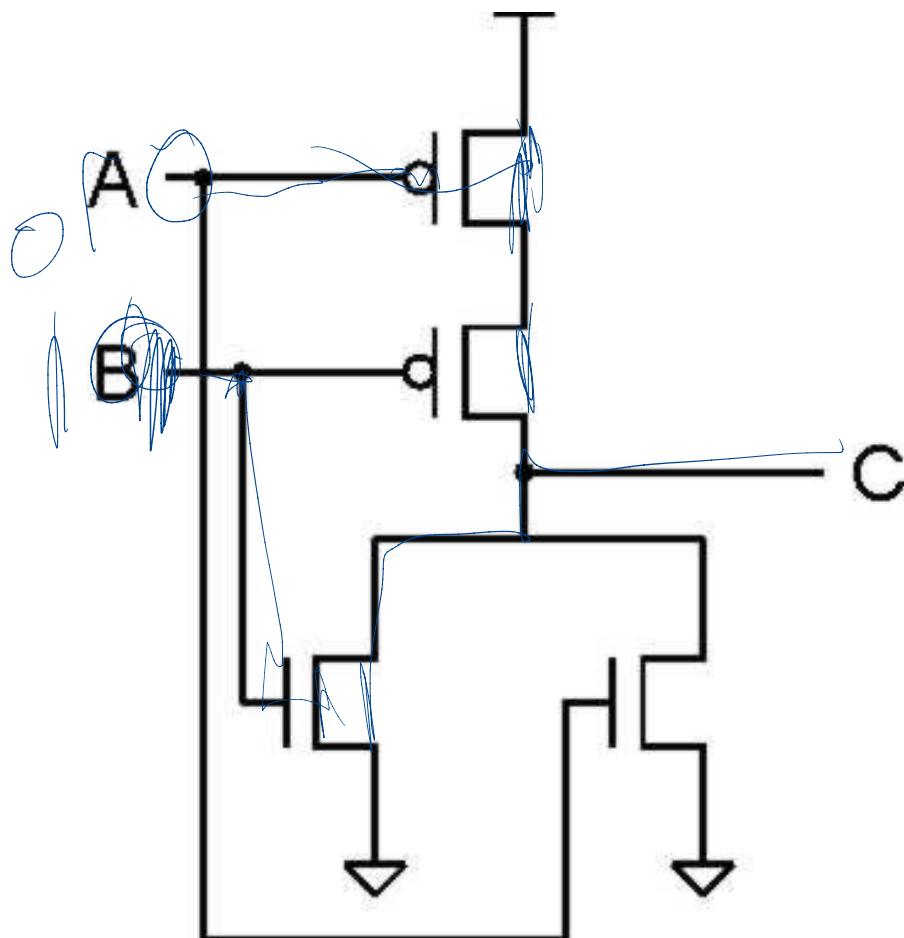

A	B	C	$A \odot B$
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

Note: Serial structure on top, parallel on bottom.


OR Gate

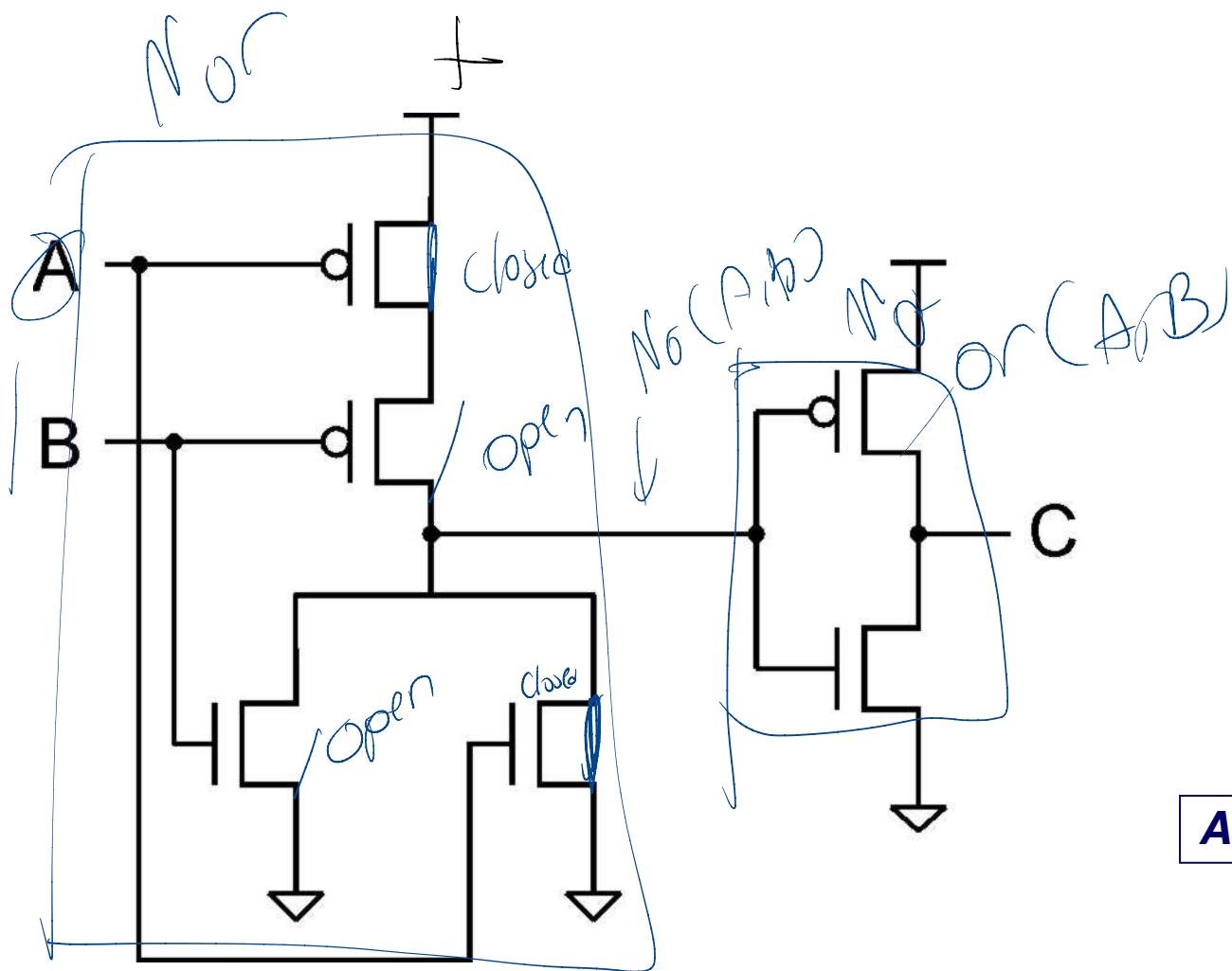


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Add inverter to NOR.


NAND Gate (AND-NOT)

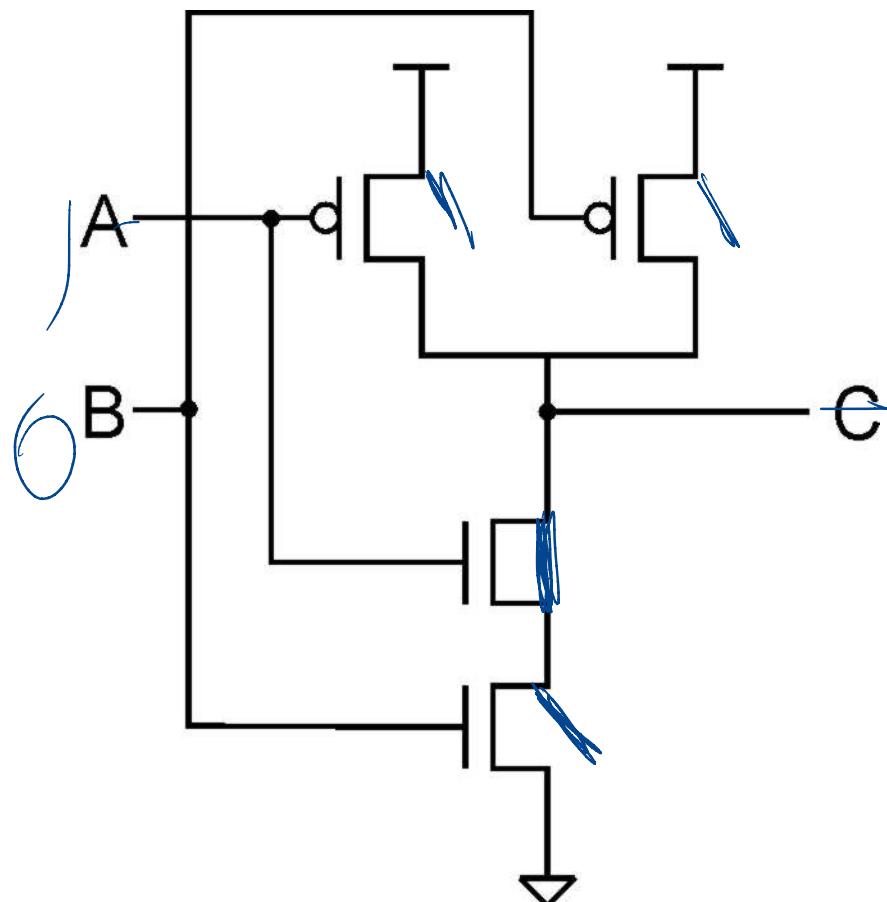

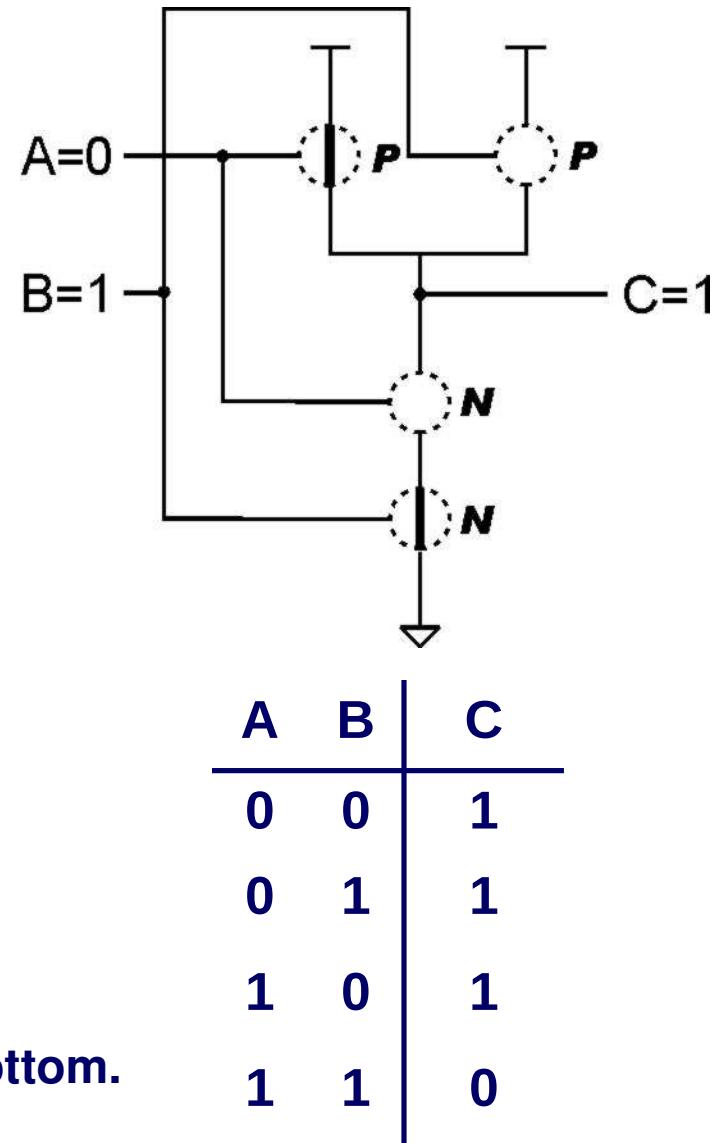Note: Parallel structure on top, serial on bottom.




AND Gate

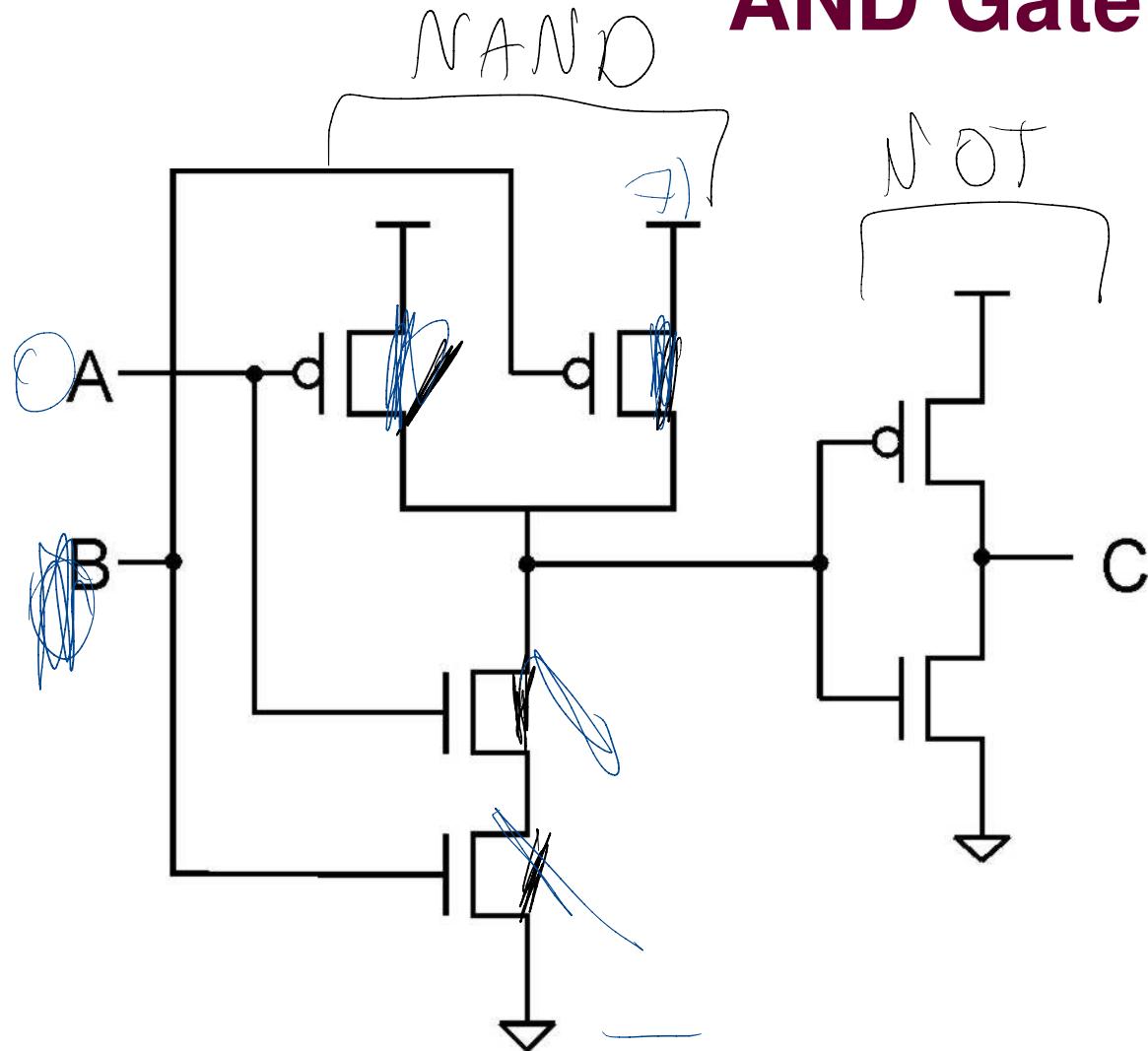

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


Add inverter to NAND.

What is this?

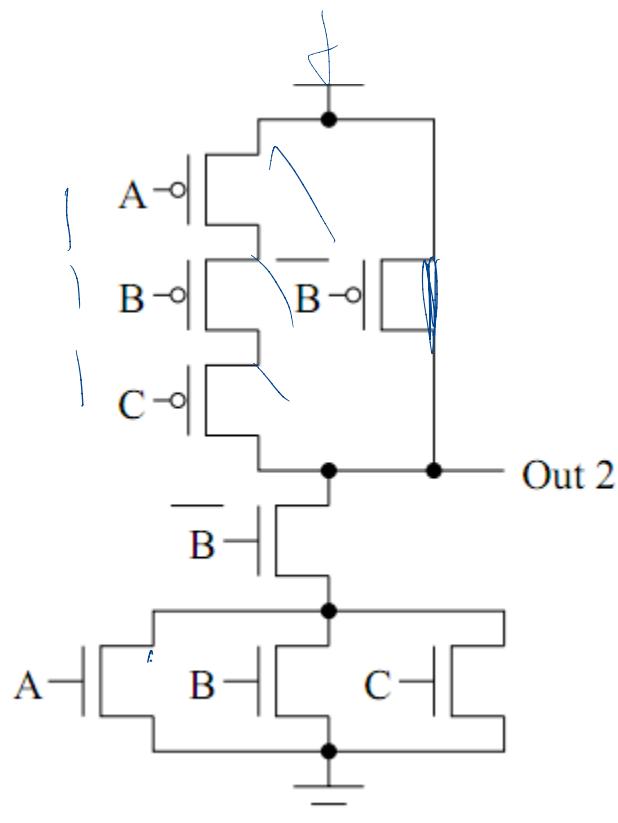


A	B	C	Out
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Basic Logic Gates Symbols

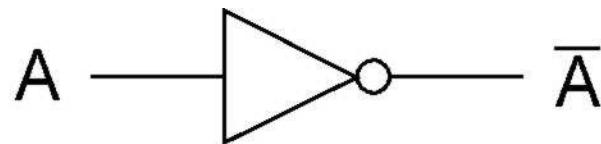


NOT

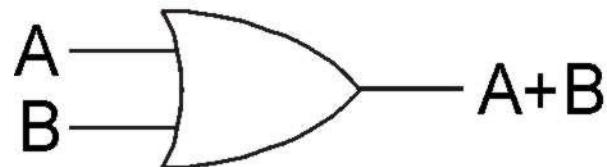


OR

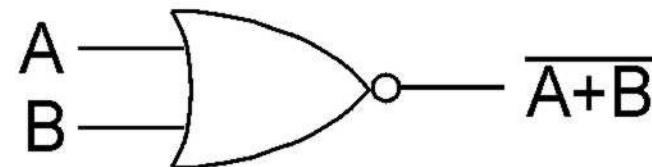

NOR

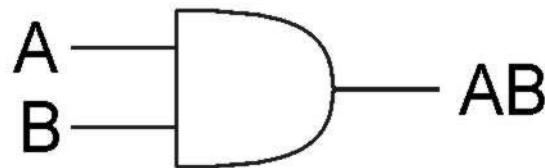

AND

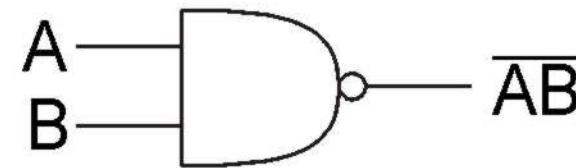


NAND

More than 2 Inputs?

AND/OR can take any number of inputs.

- AND = 1 if all inputs are 1.
- OR = 1 if any input is 1.
- Similar for NAND/NOR.

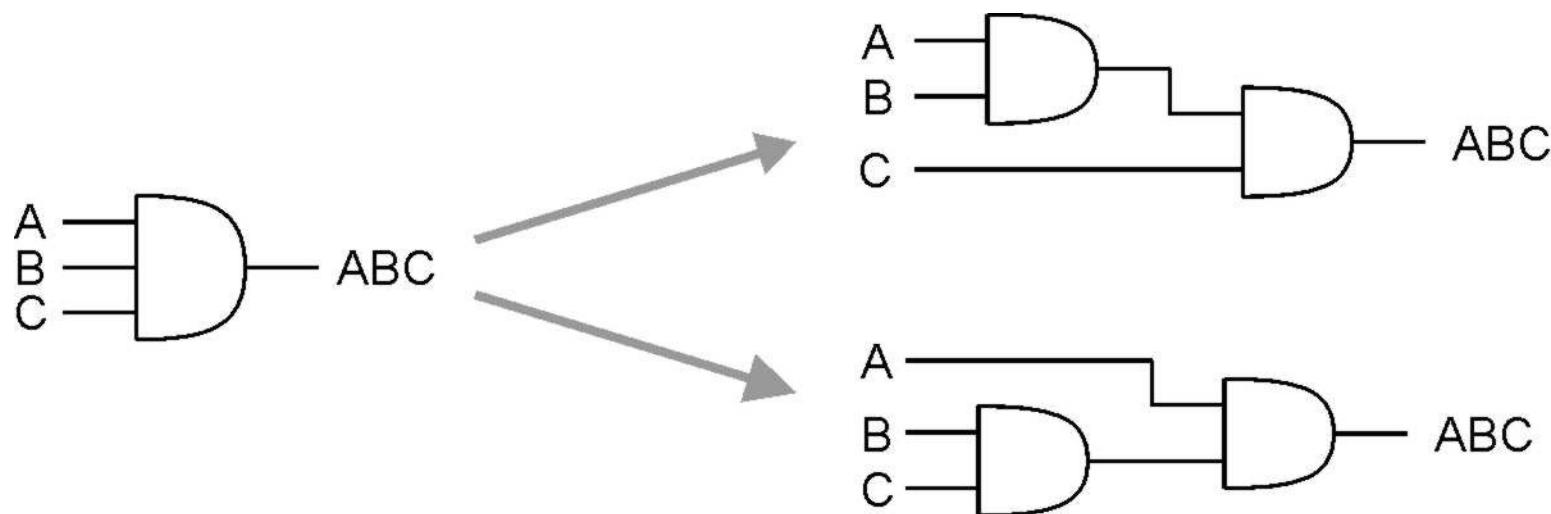
Can implement with multiple two-input gates.



Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

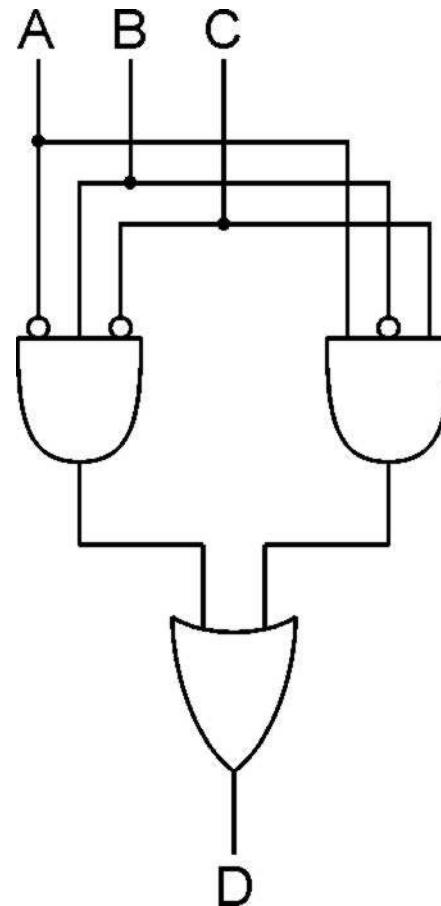


. AND combinations
that yield a "1" in the
truth table.

2. OR the results
of the AND gates.

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

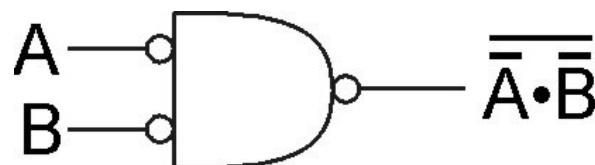

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\overline{A \cdot B}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as $A+B!$

*To convert AND to OR
(or vice versa),
invert inputs and output.*

Generally, DeMorgan's Laws:




1. $\overline{PQ} = \overline{P} + \overline{Q}$
2. $\overline{P + Q} = \overline{P} \cdot \overline{Q}$

NAND and NOR Functional Completeness

Any gate can be implemented using either NOR or NAND gates.

Why is this important?

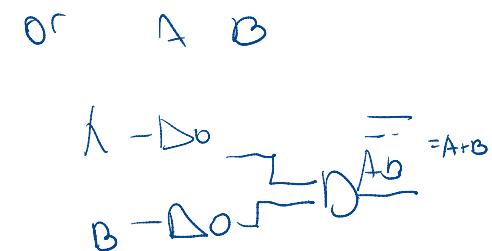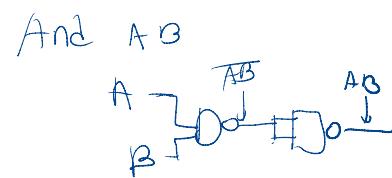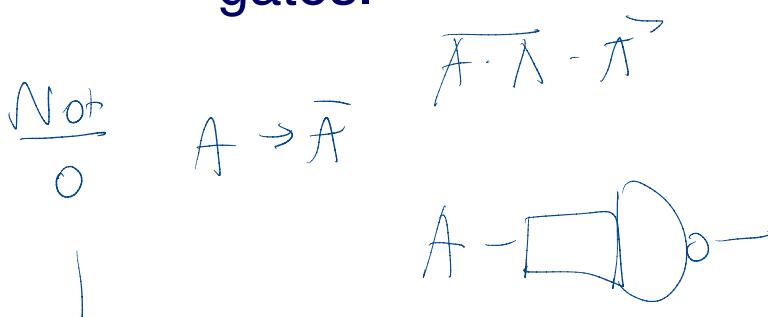- When building a chip, easier to build one with all of the same gates.



NAND, NOR universality

$$\begin{array}{ccc}
 T & F & \\
 \overbrace{\quad}^{\overbrace{A \oplus B}^{(A \oplus B)(B \oplus A)}} & \overbrace{\quad}^{\overbrace{(A \oplus B) \oplus (B \oplus A)}{(G + AB)(G' + AB')}} & F
 \end{array}$$

NAND, NOR universal because they can realize AND, OR, NOT

$$\begin{array}{c}
 (AB + \bar{A})(\bar{A}D + B) \overbrace{\bar{A} \oplus B}^A + \overbrace{\bar{A}D}^{\bar{B}} \\
 (\bar{A}B + \bar{A})(\bar{A}\bar{D} + B) \overbrace{\bar{A} \oplus B}^A + \overbrace{\bar{A}\bar{D}}^{\bar{B}}
 \end{array}$$

$\bar{A} = A \text{ NAND } A$	$\bar{A} = A \text{ NOR } A$
$AB = \overline{A \text{ NAND } B}$	$A+B = \overline{A \text{ NOR } B}$
$A+B = \overline{\bar{A} \text{ NAND } \bar{B}}$	$AB = \overline{\bar{A} \text{ NOR } \bar{B}}$

Terminology

(Boolean Algebra)

Binary variable: a symbolic representation that might be 0 or 1
(eg. X, Y, A, B)

Complement: the opposite value of variable X


Literal: a boolean variable or its complement (eg, X, \overline{X})

Expression: a set of literals combined with logical operations
(eg. AB + C)

Boolean algebra

- Values: 0, 1
- Operations: and, or, not, xor, implies, etc.
 - X AND Y: like multiplication
 - X XOR Y: like addition (mod 2)

$$A + B$$

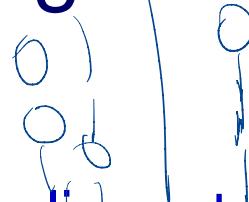

	0	1
0	0	0
1	0	1

	0	1
0	0	1
1	1	0

Boolean Identities

OR	AND	NOT	
$X+0 = X$	$X1 = X$		(identity)
$X+1 = 1$	$X0 = 0$		(null)
$X+X = X$	$XX = X$		(idempotent)
$X+\bar{X} = 1$	$\bar{X}\bar{X} = 0$		(complementarity)
		$\bar{\bar{X}} = X$	(involution)
$X+Y = Y+X$	$XY = YX$		(commutativity)
$X+(Y+Z) = (X+Y)+Z$	$X(YZ) = (XY)Z$		(associativity)
$X(Y+Z) = XY + XZ$	$X+YZ = (X+Y)(X+Z)$		(distributive)
$\overline{X+Y} = \overline{X}\overline{Y}$	$\overline{XY} = \overline{X} + \overline{Y}$		(DeMorgan's theorem)

$$\cancel{X} + \cancel{X}\cancel{Z} + \cancel{X}\cancel{Y} + \cancel{Y}\cancel{Z}$$

Boolean Algebra Example

$$F = \overline{X}YZ + \overline{X}Y\overline{Z} + XZ$$

$$\overline{X}Y(Z + \overline{Z}) + XZ \quad (\text{by reverse distribution})$$

$$\overline{X}Y + XZ \quad (\text{by complementarity})$$

$$\overline{X}Y + XZ \quad (\text{by identity})$$

Boolean Algebra Example 2

Find the complement of F

$$\begin{aligned} F &= AB + \bar{A}\bar{B} \\ \bar{F} &= \overline{AB + \bar{A}\bar{B}} \end{aligned}$$

$(\bar{A}\bar{B})(\bar{\bar{A}}\bar{B})$
 $(\bar{A} + B)(A + \bar{B})$

$(\overline{AB})(\overline{\bar{A}\bar{B}})$ (by DeMorgan's)
 $(\bar{A} + \bar{B})(\bar{\bar{A}} + \bar{B})$ (by DeMorgan's)
 $(\bar{A} + B)(A + \bar{B})$ (by involution)

Using DeMorgan's Laws to Complement

1. Big bar over AND and OR of 2 or more functions
2. Replace AND with OR, OR with AND
3. 1 with 0, 0 with 1
4. F with not(F), not(F) with F

$$\begin{aligned} & A\bar{B}C + \bar{A}CD + \bar{B}\bar{C} \\ & (\bar{A}\bar{B}C)(\bar{A}CD)(\bar{B}+\bar{C}) \\ & \overline{\bar{ABC} + \bar{ACD} + \bar{BC}} \end{aligned}$$

$$= (\bar{A}\bar{B}C)(\bar{ACD})(\bar{B}\bar{C})$$

$$= (\bar{A}\bar{B}CD)(\bar{B}+\bar{C})$$

$$= \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D}$$

$$= \bar{A}\bar{B}CD$$

$$F = \overline{\bar{ABC}}, G = \overline{\bar{ACD}}, H = \bar{B}\bar{C}, \overline{F+G+H} = \overline{\bar{F}\bar{G}\bar{H}}$$

$$(\bar{ABC})(\bar{ACD}) = \bar{ABC}D, F = B, G = \bar{C}, \overline{FG} = \overline{F+G}$$

Duals


All boolean expressions have duals

Any theorem you prove, you can also prove for the dual

To form a dual

1. replace AND with OR, OR with AND
2. replace 1 with 0, 0 with 1

Complements and Duals

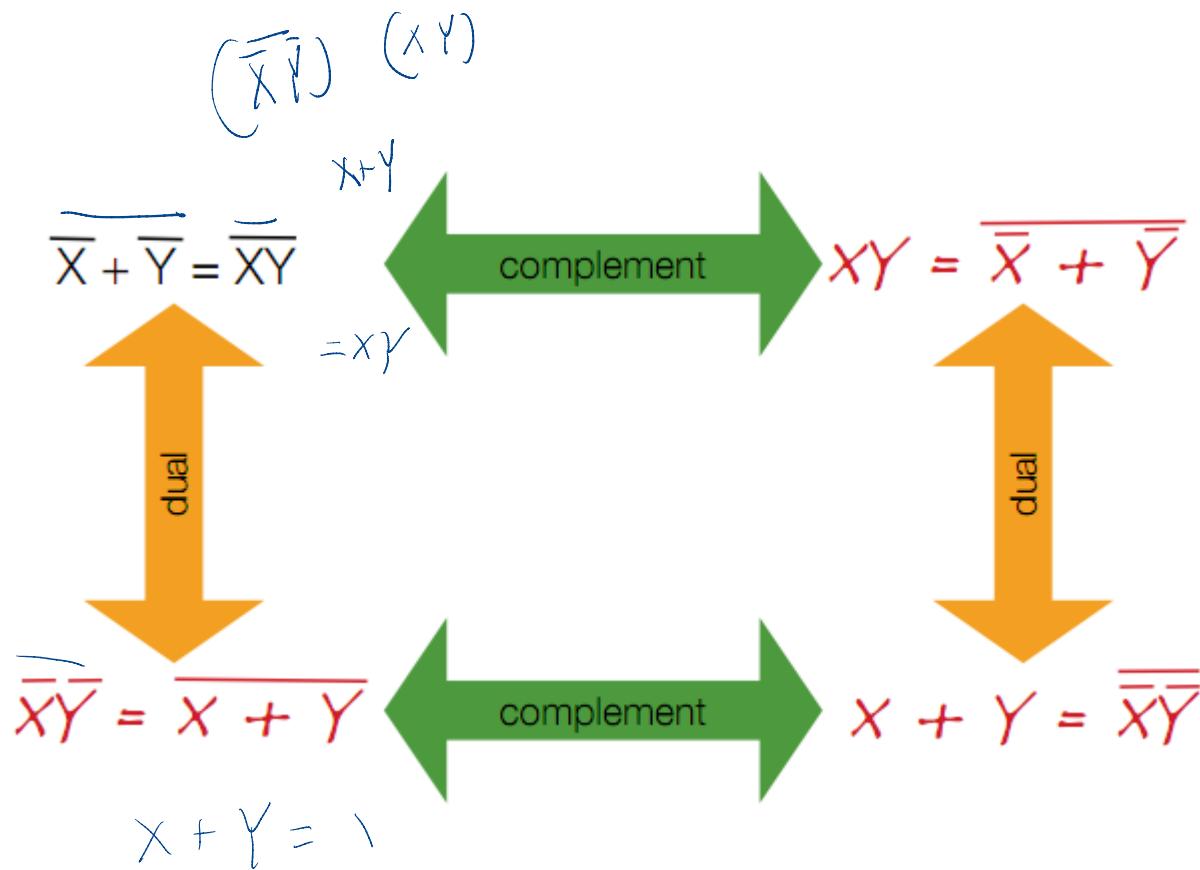

Complement Using Duals

$$A(Z + \bar{X}(YW))$$

Get dual and then complement each literal

$$(\bar{X})(Z + \bar{X}Y) (\bar{Y} + ZW)$$

)

$$F = \bar{X} + \overbrace{A(Z + \bar{X}(Y + W))} + \overbrace{\bar{Y}(Z + W)}$$

$$(X)(\bar{A} + \bar{Z}(\bar{X} + \bar{Y}\bar{W})(\bar{Y} + \bar{Z}\bar{W}))$$

$$\text{Dual: } F_{\text{dual}} = X(A + Z(\bar{X} + YW)(\bar{Y} + ZW))$$

$$\bar{F} = \bar{X}(\bar{A} + \bar{Z}(X + \bar{Y}\bar{W})(Y + \bar{Z}\bar{W}))$$

Simplifying Expressions

$$\begin{aligned}
 & \bar{A}BC + A\bar{B}C + AB(C+C) \\
 & \bar{A}BC + A\bar{B}C + A\bar{B} \\
 & \bar{A}BC + A(\bar{B}C + B) \\
 & \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \\
 & \downarrow \quad \bar{A}BC + A(B+C) \\
 & \quad \quad \quad \bar{A}BC + AB + AC \\
 & BC(\bar{A} + A) + A\bar{B}C + AB\bar{C} \\
 & \quad \quad \quad B(\bar{A}(C+A)+AC) \\
 & \quad \quad \quad B(A+1)+AC \\
 & \quad \quad \quad B + AC \\
 & \downarrow \quad BC(1) + A\bar{B}C + AB\bar{C} \\
 & BC + A\bar{B}C + AB\bar{C} \\
 & \quad \quad \quad B(C + A\bar{C}) + A\bar{B}C \\
 & \quad \quad \quad B(C + A\bar{C}) + A\bar{B}C \\
 & \quad \quad \quad (\bar{C})(C+C) \\
 & \quad \quad \quad f \bar{A}C
 \end{aligned}$$

$$B(C + A) + A\bar{B}C$$

$$BC + AB + A\bar{B}C$$

$$BC + A(B + \bar{B}C)$$

$$BC + A(B + C)$$

$$BC + AB + AC$$

$$C+A(C+\bar{C}) \\ C+A(1) \Rightarrow C + A$$

$$(B - \bar{B})(B + C)$$

$$B + \bar{B}L + \bar{B}\bar{C}$$

$$B + C(B + \bar{B})$$

$$\text{Heart} + C$$